Comparing functional Embedded Domain-Specific Languages for hardware description

João Paulo Pizani Flor

Department of Information and Computing Sciences, Utrecht University

February 13th, 2014

Motivation
Hardware EDSLs

Chosen EDSLs
Evaluation criteria

ALU
Memory bank

Analysis of the EDSLs
Lava
ForSyDe

orSyDe oquet



Table of Contents

Introduction

Motivation Hardware EDSLs

Analyzed EDSLs

Chosen EDSLs Evaluation criteria

Modeled Circuits

ALU Memory bank **CPU**

Analysis of the EDSLs

Lava ForSyDe Coquet

Conclusions

Hardware EDSLs

ALLI



Section 1

Introduction

Introduction

Motivation Hardware EDSIs

Chosen EDSLs

Evaluation crite

ALU Memory bank

Analysis of the EDSLs

ForSyDe Coquet



Hardware design

Hardware design is very complex and very expensive:

- ▶ Mistakes discovered after sales are much more serious
 - No such thing as an "update" to a chip
- ▶ Thus the need for extensive simulation
 - Sometimes even exhaustive simulation
 - Using specific and expensive systems
- ► The downfall of *Moore's Law* doesn't help either
 - More need for parallelism, fault-tolerance, etc.
 - Design even more error-prone and validation even more complex

Introduction

Motivation Hardware EDS

Analyzed EDSLs Chosen EDSLs

Modeled Circuit ALU Memory bank

Analysis of the EDSLs

orSyDe oquet



Hardware design

- ▶ The level of abstraction has been lifted already...
 - VHDL in the 1980s
- Functional languages suggested for hardware design, also since the 1980s
 - First, languages designed from scratch
 - Then, embedded in general-purpose functional languages

Motivation

Motivation Hardware EDSI

Analyzed EDSLs
Chosen EDSLs

Modeled Circuits

Memory bank CPU

EDSLs Lava ForSyDe

orSyDe oquet



Goals of this project

Motivation

ALU

Lava



Domain-Specific Languages

A computer language (turing-complete or *not*) targeting a specific application domain.

Example DSLs:

- SQL (database queries)
- CSS (document formatting)
- MATLAB (Matrix programming)
- VHDL (Hardware description)

Motivation

Hardware EDSLs

Chosen EDSLs

Modeled Circuit

Memory bank CPU

EDSLs Lava ForSyDe

oquet



Domain-Specific Languages

A computer language (turing-complete or *not*) targeting a specific application domain.

Example DSLs:

- SQL (database queries)
- CSS (document formatting)
- MATLAB (Matrix programming)
- VHDL (Hardware description)

A DSL can also be *embedded* in a general-purpose language.

Example EDSLs:

- ▶ Boost.Proto (C++ / parser combinators)
- Diagrams (Haskell / programmatic drawing)
- Parsec (Haskell / parser combinators)

Hardware EDSLs

ALLI



Example of an EDSL: Parsec

A simple parser for a "Game of Life"-like input format:

```
dead, alive :: Parser Bool
dead = fmap (const False) (char '.')
alive = fmap (const True) (char '*')
line :: Parser [Bool]
line = many1 (dead <|> alive)
board :: Parser [[Bool]]
board = line 'endBy1' newline
parseBoardFromFile :: FilePath -> IO [[Bool]]
parseBoardFromFile filename = do
    result <- parseFromFile board filename
    return $ either (error . show) id result
```

Hardware EDSLs
Analyzed EDSLs
Chosen EDSLs
Evaluation criteria
Modeled Circuit
ALU
Memory bank
CPU
Analysis of the
EDSLs
Lava
ForSvDe



Hardware EDSLs

An EDSL used for hardware design-related tasks. Can encompass:

- Modeling / description
- Simulation (validation)
- Formal verification
- Synthesis to other (lower-level) languages

Example of a hardware EDSL (Lava):

Motivation

Hardware EDSLs

Chosen EDSLs

Modeled Circuit

Memory bank CPU

EDSLs Lava ForSyDe



Section 2

Analyzed EDSLs

Introduction Motivation

Hardware ED

Analyzed EDSLs

Chosen EDSLs Evaluation criteria

ALU ALU

Memory bank CPU

Analysis of the EDSLs

orSyDe oquet



Choice criteria

Introduction

Motivation Hardware EDSLs

Analyzed EDSLs

Chosen EDSLs Evaluation criteria

Modeled Circui ALU Memory bank

Analysis of the EDSLs



Chosen EDSLs

The language we chose to evaluate, with the respective host language, were:

- ▶ Lava (Haskell chalmers-lava dialect)
- ForSyDe (Haskell)
- Coquet (Coq interactive theorem prover)

Motivation
Hardware EDSLs

Analyzed EDSLs

Chosen EDSLs Evaluation criteria

Modeled Circuits
ALU
Memory bank

Analysis of the EDSLs Lava

Coquet



Evaluation criteria

- Simulation
- Verification
- Genericity
- Depth of embedding
- ▶ Tool integration
- Extensibility

Motivation
Hardware EDSLs

Chosen FDSI s

Evaluation criteria

Modeled Circuit ALU Memory bank

Analysis of the EDSLs

Lava ForSyDe Coquet



Section 3

Modeled Circuits

Introduction Motivation

Motivation Hardware EDSLs

Chosen EDSLs

Modeled Circuits

ALU Memory bank

Analysis of the EDSLs Lava

> ForSyDe Coquet



Choice criteria

- ▶ Not too simple, not too complex
- ► Familiar to any hardware designer
 - No signal processing, etc.
- Well-defined, pre-specification
 - · Results to verify the models against

Motivation
Hardware EDSLs

Chosen EDSLs

Modeled Circuits

ALU Memory bank CPU


Analysis of the EDSLs Lava

Loquet



Chosen circuits

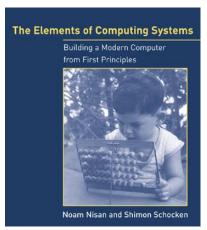We cherry-picked circuits from the book "Elements of Computing Systems", as they satisfied all of our demands.



Motivation
Hardware EDSLs

Chosen EDSLs
Evaluation criteria

Modeled Circuits

ALU Memory bank CPU

Analysis of the EDSLs Lava

ForSyDe Coquet

Conclusions

Figure: "Elements of Computing Systems" - Nisan, Schocken, available at http://www.nand2tetris.org.



Universiteit Utrecht

Chosen circuits

Circuit 1 A 2-input, 16-bit-wide, simple ALU Circuit 2 A 64-word long, 16-bit wide memory block Circuit 3 An extremely reduced instruction set CPU, the

Hack CPU.

Let's take a quick look at each of these circuit's specification. . .

Modeled Circuits

ALU



Circuit 1: ALU

Some of the circuit's key characteristics:

- ▶ 2 operand inputs and 1 operand output, each 16-bit wide
- ▶ 1 output flag
- Can execute 18 different functions, among which:
 - Addition, subtraction
 - Bitwise AND / OR
 - Constant outputs
 - · Addition of constants to an operand
 - Sign inversion

Motivation
Hardware EDSLs

Chosen EDSLs
Evaluation criteria

ALU

Memory bank CPU

Analysis of the EDSLs Lava

orSyDe Coquet



Circuit 1: block diagram

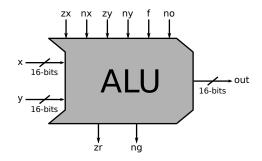


Figure: Input/Output ports of circuit 1, the ALU.

Introduction

Motivation

Hardware EDSLs

Chosen EDSLs
Evaluation criteria

ALU

Memory bank CPU

Analysis of the EDSLs
Lava
ForSyDe



Circuit 1: specification

The behaviour of the ALU is specified by the values of the *control bits* and *flags*:

```
zx and zy Zeroes the "x" and "y" inputs, respectively nx and ny bitwise negation on the "x" and "y" inputs f Selects the function to be applied: "f" = 1 for addition, "f" = 0 for bitwise AND no bitwise negation on the output ALU output zr and ng The output flag "zr" = 1 iff the ALU output is zero. "ng" = 1 iff the output is negative.
```

Formal definition and test cases in the book.

Motivation
Hardware EDSLs
Analyzed EDSL
Chosen EDSLs
Evaluation criter
Modeled Circu
ALU
Memory bank
CPU
Analysis of the
EDSLs
Lava
ForSyDe
Conuet



Circuit 2: RAM64

Some of the circuit's key characteristics:

- ► Sequential circuit, with clock input
- ▶ 64 memory words stored, each 16-bit wide
- ▶ Address port has width log₂ 64 = 6 bit

Introduction

Motivation

Hardware EDSLs

Chosen EDSLs

Modeled Circuit

Memory bank CPU

Analysis of the EDSLs
Lava

oquet



Circuit 2: block diagram

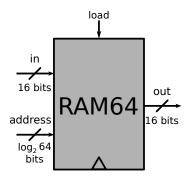


Figure: Input/Output ports of circuit 2, the RAM64 block.

Motivation
Hardware EDSLs
Analyzed EDSLs
Evaluation criteria
Modeled Circuit
ALU
Memory bank
CPU
Analysis of the
EDSLs
Lava
ForSyDe
Coquet



Circuit 2: specification

- ► The output "out" holds the value at the memory line indicated by "address".
- ► Iff "load" = 1, then the value at input "in" will be loaded into memory line "address".
- ► The loaded value will be emitted on "out" at the *next* clock cycle.

Introduction

Motivation

Hardware EDSLs

Chosen EDSLs
Evaluation criteria

Modeled Circuit

ALU

Memory bank

Analysis of the EDSLs

orSyDe oquet



Circuit 3: Hack CPU

- A very reduced instruction set CPU
 - Only 2 instructions: "C" and "A"
- ► Follows the Harvard architecture
 - Separate address spaces for data and instruction memory.
- Instructions are 16-bits wide
 - · As well as the memory input and output
- ► Two internal registers: "D" and "A"

Motivation
Hardware EDSLs

Chosen EDSLs

Modeled Circuit

ALU Memory bank CPU

Analysis of the EDSLs Lava ForSyDe

.....



Circuit 3: block diagram

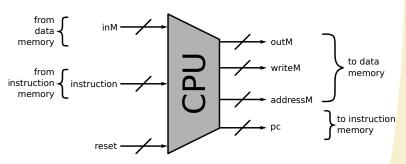


Figure: Input/Output ports of circuit 3, the Hack CPU.


Introduction
Motivation
Hardware EDSLs
Analyzed EDSLs
Chosen EDSLs
Evaluation criteria
Modeled Circuits
ALU
Memory bank
CPU
Analysis of the
EDSLs
Lava



Circuit 3: specification

Circuit 3 runs "A" and "C" instructions, according to the *Hack* assembly specification.

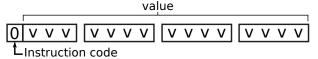► The "A" instruction: sets the "A" register.



- ▶ The value in "A" can be used:
 - As operand for a subsequent computation
 - As address for jumps

Introduction

Motivation

Hardware EDSLs

Analyzed EDSLs
Chosen EDSLs

Modeled Circuits
ALU
Memory bank

CPU Analysis of t

> ava orSyDe

Conclusions

Universiteit Utrecht

Circuit 3: specification

Circuit 3 runs "A" and "C" instructions, according to the *Hack* assembly specification.

► The "C" instruction: sets the "C" register, performs computation or jumps.

| | comp | dest | jump |
|--------------|------------------|------------|----------|
| | • | · · | |
| 1 x x a | c1 c2 c3 c4 c5 c | 6 d1 d2 d3 | j1 j2 j3 |
| Linstruction | code | | |

- Some peculiarities:
 - Bits "c1" to "c6" control the ALU
 - · conditional or unconditional jumps
 - destination of the computation result: "A", "D", "M"

Introduction

Motivation

Hardware EDSLs

Chosen EDSLs
Evaluation criteria

Modeled Circuits
ALU
Memory bank

CPU Analysis of tl

> ava orSyDe



Circuit 3: specification (parts)

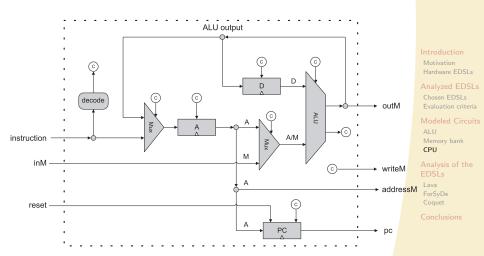


Figure: Parts used to build the *Hack* CPU, and their interconnection.



Section 4

Analysis of the EDSLs

Introduction Motivation

Hardware EDSL

Chosen EDSLs

Evaluation criteria

ALU Memory bank

Analysis of the EDSLs

Lava ForSyDe Coquet



Lava

- Developed at Chalmers University of Technology, Sweden
 - Initially by Koen Claessen and Mary Sheeran
 - Later also Per Bjesse and David Sands
- Has several dialects
 - chalmers-lava, xilinx-lava, kansas-lava, etc.
 - We focus on the "canonical" chalmers-lava

ntroduction Motivation Hardware EDSLs

Chosen EDSLs Evaluation criteria

Modeled Circuits
ALU
Memory bank

Analysis of the

Lava ForSyDe



Lava's key characteristics

- Deep-embedded
- Observable sharing
 - "Type-safe pointer equality" to detect sharing and recursion
 - Advantages and disadvantages clearer with examples
- Capable of simulation, verification and synthesis
 - Generates flat VHDL
 - External tools for verification
- Very "functional" style of hardware description
 - Will become clearer with examples

Introduction

Motivation

Hardware EDSLs

Chosen EDSLs

Modeled Circuits
ALU

CPU
Analysis of the

EDSLs Lava

orSyDe Coquet



Lava: Adders

```
type SB = Signal Bool
halfAdder :: (SB, SB) -> (SB, SB)
halfAdder inputs = (xor2 inputs, and2 inputs)
fullAdder :: (SB, (SB, SB)) -> (SB, SB)
fullAdder (cin, (a, b)) = (s, cout)
   where
      (ab, c1) = halfAdder (a, b)
      (s, c2) = halfAdder (ab, cin)
     cout = or2 (c1, c2)
rippleCarryAdder :: [(SB, SB)] -> [SB]
rippleCarryAdder ab = s
   where (s, _) = row fullAdder (low, ab)
```

- Straightforward Haskell constructs
- "and2", "xor2", etc. are Lava's atomic circuits

Introduction

Motivation

Hardware EDSLs

Chosen EDSLs

Modeled Circuit
ALU
Memory bank

Analysis of the

Lava ForSyDe

Conclusions

Universiteit Utrecht

Lava: Simulation and verification

A taste of simulation in Lava:

- Cannot be easily automated: equality of Signal is non-trivial
- And verification...

```
prop_FullAdderCommutative :: (SB, (SB, SB)) -> SB
prop_FullAdderCommutative (c, (a, b)) =
  fullAdder (c, (a, b)) <==> fullAdder (c, (b, a))
```

-- satzoo prop_FullAdderCommutative

- Advantage: Used in conjunction with an external SAT solver (e.g. Satzoo)
- Disadvantage: Only verifies instances of specific size

Introduction

Motivation

Hardware EDSLs

Chosen EDSLs

Modeled Circuits
ALU
Memory bank

Analysis of the

Lava ForSyDe Coquet

onclusions.

Universiteit Utrecht

Lava: ALU

```
type ALUControlBits = (SB, SB, SB, SB, SB, SB, SB)
alu :: ([SB], [SB], ALUControlBits) -> ([SB], SB, SB)
alu (x, y, (zx, nx, zy, ny, f, no)) = (out', zr, ng)
   where x' = mux (zx, (x, replicate (length x) low))
               = mux (nx, (x', map inv x'))
          ٧,
                = mux (zy, (y, replicate (length x) low))
          v'' = mux (ny, (y', map inv y'))
         out
               = let xv'' = zip x'' v''
                  in mux (f, (andl xy'', adder xy''))
         out'
                = mux (no, (out, map inv out))
                = foldl (curry and2) low out'
          zr
                = equalBool high (last out')
          ng
          adder = rippleCarryAdder
```

Motivation
Hardware EDSLs
Analyzed EDSL
Chosen EDSLs
Evaluation criteri
Modeled Circui
ALU
Memory bank
CPU
Analysis of the

Lava

Remarks

- Cannot introduce new, meaningful datatypes
 - Only Signal Bool is synthesizable
 - Or tuples/lists thereof
- ▶ Input/Output types have to be *uncurried*
- Weak type-safety over the inputs/outputs
 - Working with tuples is tiresome and has limitations
 - Lists don't enforce size constraints

Motivation
Hardware EDSLs

Chosen EDSLs

Modeled Circuit
ALU
Memory bank

Analysis of the

Lava ForSyDe Coquet



Lava: RAM64

```
reg :: (SB, SB) -> SB
reg (input, load) = out
    where dff = mux (load, (out, input))
          out = delay low dff
regN :: Int -> ([SB], SB) -> [SB]
regN n (input, load) = map reg $ zip input (replicate n load)
ram64Rows :: Int -> ([SB], (SB,SB,SB,SB,SB,SB), SB) -> [SB]
ram64Rows n (input, addr, load) = mux64WordN n (addr, regs)
   where memLine sel = regN n (input, sel <&> load)
                      = map memLine (decode6To64 addr)
          regs
```

Motivation
Hardware EDSLs
Analyzed EDSLs
Chosen EDSLs
Evaluation criteri
Modeled Circui
ALU
Memory bank
CPU
Analysis of the
EDSLs
Lava

Remarks

Positive:

- Uses host language for binding (let/where) and recursion
- Uses host language for structural combinators

Negative:

- Again, weak type-safety of lists
 - Extra Int parameter controls port sizes
- ▶ No modularity in the generated VHDL code.

Introduction

Motivation

Hardware EDSLs

Chosen EDSLs Evaluation criteria

Modeled Circuit
ALU
Memory bank

Analysis of the EDSLs

Lava ForSyDe Coquet

Conclusions

Lava: Hack CPU (some parts)

```
programCounter :: Int -> (SB, SB, [SB]) -> [SB]
programCounter n (reset, set, input) = out where
    incr
            = increment out
    out = delay (replicate n low) increset
    incinput = mux (set, (incr, input))
    increset = mux (reset, (incinput, replicate n low))
type Dest = (SB, SB, SB)
type JumpCond = (SB, SB, SB)
type CPUCtrl = (SB, SB, Dest, JumpCond, ALUCtrl)
instructionDecoder :: HackInstruction -> CPUCtrl
instructionDecoder (i0,_,_,i3,i4,i5,i6,i7,i8,i9,...,i15)
    = (aFlag, cAM, cDest, cJump, cALU) where
    aFlag = i0
    cAM = inv i3
    cDest = (i10, i11, i12)
    cJump = (i13, i14, i15)
    cALU = (i4, i5, i6, i7, i8, i9)
```

Introduction

Motivation

Hardware EDSIs

Analyzed EDSLs Chosen EDSLs

Modeled Circuits

CPU
Analysis of the

EDSLs

Lava ForSyDe Coquet

Conclusions

Remarks

Could benefit from:

- ► Fixed-length vectors
 - ForSyDe-style or with type-level naturals in recent GHC.
- Slicing operators over vectors
- Synthesizable user-defined datatypes

Introduction

Motivation

Hardware EDSLs

Chosen EDSLs

Modeled Circuits
ALU
Memory bank

Analysis of the

Lava ForSvDe

ForSyDe Coquet



ForSyDe

- ▶ Based on the "Formal System Design" approach
 - Royal Institute of Technology KTH, Sweden
- Available for Haskell and SystemC
- Has BOTH shallow and deep-embedded "versions"
 - Same library, subtle distinction
 - · Will become clearer with examples
- ► Template Haskell to express circuits with Haskell syntax

Motivation
Hardware EDSLs

Chosen EDSLs
Evaluation criteria

Modeled Circuits
ALU
Memory bank

Analysis of the EDSLs

Lava ForSyDe

orSyDe



ForSyDe's key concepts

- Models of Computation (MoCs)
 - We focus on the synchronous MoC
- Processes
 - A process belongs to a MoC
 - Built with a process constructor
- Signals
 - Connections among processes

Motivation
Hardware EDSLs

Chosen EDSLs Evaluation criteria

Modeled Circuit
ALU
Memory bank


Analysis of the EDSLs

Lava ForSvDe

Coquet



ForSyDe's key concepts

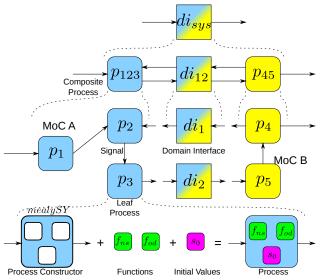

Motivation
Hardware EDSLs

Analyzed EDSLs Chosen EDSLs

Modeled Circuit

ALU Memory bank CPU

Analysis of the EDSLs Lava ForSvDe

orSyDe Coquet

Conclusions



ForSyDe: ALU (non-synth)

```
type S = Signal
type Word = Int16
data ALUOp = ALUSum | ALUAnd
    deriving (Typeable, Data, Show)
$(deriveLift1 ''ALUOp)
type ALUCtrl = (Bit, Bit, Bit, Bit, ALUOp, Bit)
type ALUFlag = (Bit, Bit)
bo, bb :: Bit -> Bool
bo = bitToBool
bb = boolToBit
```

Introduction

Motivation

Hardware EDSLs

Chosen EDSLs

Modeled Circuits
ALU
Memory bank

Memory bank CPU

EDSLs
Lava
ForSyDe
Coquet



ForSyDe: ALU (non-synth)

```
aluFunc :: ProcFunc (ALUCtrl -> Word -> Word -> (Word, ALUFlag)) Introduction Mativation
aluFunc = $(newProcFun [d]
  aluFunc' (zx,nx,zy,ny,f,no) x y =
      (out, (bb (out == 0), bb (out < 0)))
    where
      zfzw = if bo z then 0 else w
                                                                   ALLI
      nf n w = if bo n then complement welse w
      (xn, yn) = (nf nx \$ zf zx \$ x, nf ny \$ zf zy \$ y)
      out
              = nf no $ case f of
                                                                   Lava
                           ALUSum -> xn + yn
                                                                   ForSvDe
                           ALUAnd -> xn .&. yn |] )
```

```
aluProc :: S ALUCtrl -> S Word -> S (Word,ALUFlag)
aluProc = zipWith3SY "aluProc" aluFunc
```

ForSyDe: synthesis restrictions

Restrictions imposed on a model by ForSyDe so that it can be translated to VHDL:

- ProcFun-related:
 - Limited argument types (instances of ProcType)
 - Int, Int8, ..., Bool, Bit
 - Enumerated types (deriving Data and Lift)
 - Tuples and FSVec's
- VHDL engine-related:
 - No point-free notation
 - Single clause / no pattern matching
 - No where or let bindings

ALLI

ForSvDe



ForSyDe: ALU (synthesizable)

```
zProc :: ProcId -> S Bit -> S Word -> S Word
zProc name = zipWithSY name $(newProcFun [d|
    f :: Bit -> Word -> Word
    f z w = if z == H then 0 else w | 1)
nProc :: ProcId -> S Bit -> S Word -> S Word
nProc name = zipWithSY name $(newProcFun [d])
    f :: Bit -> Word -> Word
    f n w = if n == H then negate w else w | ])
compProc :: S Bit -> S Word -> S Word -> S Word
compProc = zipWith3SY "compProc" $(newProcFun [d|
    f :: Bit -> Word -> Word -> Word
    f \circ x y = if \circ == H \text{ then } x + y \text{ else } x \cdot \&. y \mid ]
tzProc :: S Word -> S Bit ...
```

Motivation Hardware EDSLs Analyzed EDSLs Chosen EDSLs Evaluation criteri Modeled Circui ALU Memory bank CPU Analysis of the EDSLs Lava ForSyDe



tnProc :: S Word -> S Bit

ForSyDe: ALU (synthesizable)

Motivation Hardware EDSL Analyzed EDSL Chosen EDSLs Evaluation crite Modeled Circo ALU Memory bank CPU Analysis of the EDSLs Lava ForSyDe



ForSyDe: Muxes

```
mux2 :: S Bit -> S Word -> S Word -> S Word
mux2 = zipWith3SY "zipWith3SY" $(newProcFun [d]
  f s x y = if s == L then x else y | ])
mux2SysDef :: SysDef (S Bit -> S Word -> S Word -> S Word)
mux2SysDef = newSysDef mux2 "mux2" ["s","i1","i2"] ["o"]
mux4 :: S (FSVec D2 Bit) -> S (FSVec D4 Word) -> S Word
mux4 ss is = (mux2' "m1") (sv ! d1) m00 m01 where
  mux2' 1 = instantiate 1 mux2SysDef
          = unzipxSY "unzipSel" ss
  SV
  iv
          = unzipxSY "unzipInp" is
  mOO
          = (mux2' "m00") (sv ! d0) (iv ! d0) (iv ! d1)
  m01
          = (mux2' "m01") (sv ! d0) (iv ! d2) (iv ! d3)
mux4SysDef :: SysDef ( S (FSVec D2 Bit) -> S (FSVec D4 Word)
                    -> S Word)
mux4SysDef = newSysDef mux4 "mux4" ["s","is"] ["o"]
```

Introduction

Motivation

Hardware EDSLs

Analyzed EDSLs
Chosen EDSLs

Modeled Circuits
ALU
Memory bank
CPII

Analysis of the EDSLs Lava ForSyDe

oquet

onclusions

Remarks

Positive:

- Generated VHDL is very modular
 - One VHDL entity per ForSyDe component
 - Good for tool integration

Negative:

- Interface "conflicts" caused by FSVec and process constructors
 - "zip-unzip" pattern

Motivation Hardware EDSLs

Chosen EDSLs

Modeled Circuits
ALU
Memory bank

CPU
Analysis of the

EDSLs Lava ForSyDe Coquet



ForSyDe: RAM64

```
reg :: S Word -> S Bit -> S Word
reg input load = out where
    out = delaySY "delay" (0 :: WordType) dff
                                                               Hardware EDSLs
    dff = (instantiate "mux2" mux2SysDef) load out input
ram64 :: S Word -> S (FSVec D6 Bit) -> S Bit -> S Word
ram64 input addr load = mux' addr (zipxSY "zipRows" rs) where
                                                               ALLI
 mux'
        = instantiate "mux" mux64SysDef
  decoder' = instantiate "decoder" decode6To64SysDef
  reg' l = instantiate l regSysDef
 and' l = instantiate l andSysDef
                                                               Lava
                                                               ForSvDe
  r(s,l) = (reg' l) input ((and' (l ++ ":and")) load s)
  rs'
          = unzipxSY "unzipAddr" $ decoder' addr
          = V.map r $ V.zip rs' (V.map (\n -> "r" ++ show n)
  rs
                                 (V.unsafeVector d64 [0..63]))
```

ram64SysDef = newSysDef ram64 "ram64" ["i", "a", "l"] ["o"]

Remarks

- ► Component instantiation
 - Introduces hierarchy in the design
 - Influences generated VHDL
- Manual name management
 - Error-prone
 - Every process must have a unique identifier
 - Already was a (lesser) issue with the muxes

Introduction

Motivation

Hardware EDSLs

Chosen EDSLs

Modeled Circuits
ALU
Memory bank

Analysis of the

EDSLs Lava ForSvDe

ForSyDe Coquet



ForSyDe: Hack CPU (part)

```
type HackInstruction = FSVec D16 Bit
type Dest = (Bit, Bit, Bit)
type Jump = (Bit, Bit, Bit)
instructionDecoder :: S HackInstruction
                     -> S (Bit, Bit, Dest, Jump, ALUCtrl)
instructionDecoder = mapSY "mapSYdecoder" decoderFun where
  decoderFun = $(newProcFun [d]
    f :: HackInstruction -> (Bit, Bit, Dest, Jump, ALUCtrl)
   fi = (i!d0
          , not (i!d3)
          , (i!d10, i!d11, i!d12)
          , (i!d13, i!d14, i!d15)
          , (i!d4, i!d5, i!d6, i!d7, i!d8, i!d9)
          ) [])
```

Introduction

Motivation

Hardware EDSLs

Chosen EDSLs

Modeled Circuit: ALU Memory bank

Analysis of the EDSLs

ForSyDe Coquet



Coquet

- Developed by Thomas Braibant (INRIA, France)
 - Seminal paper published in 2011
- ► Library embedded in the *Coq* proof assistant
 - Deep-embedded
 - Models the architecture of circuits
- Allows for correctness proofs of circuits
 - According to a given specification
 - Provides tactics to help with these proofs
 - More powerful, inductive proofs

ALLI

Coquet



Coquet: The Circuit type

```
Context {tech : Techno}
Inductive Circuit: Type -> Type -> Type :=
| Atom : forall {n m : Type} {Hfn : Fin n} {Hfm : Fin m},
             techno n m -> Circuit n m
 Plug : forall {n m : Type} {Hfn : Fin n} {Hfm : Fin m}
            (f : m -> n), Circuit n m
 Ser : forall {n m p : Type},
             Circuit n m -> Circuit m p -> Circuit n p
 Par : forall {n m p q : Type},
             Circuit n p -> Circuit m q
             \rightarrow Circuit (n + m) (p + q)
 Loop: forall {n m p : Type},
             Circuit (n + p) (n + p) -> Circuit n m
```

Introduction

Motivation

Hardware EDSLs

Chosen EDSLs
Evaluation criteria

Modeled Circuit ALU Memory bank

Analysis of the EDSLs
Lava
ForSyDe

Coquet

Conclusions

onclusions



Features from the Circuit type

- Circuit structure as constructors of the datatype
 - Explicit loops (recursion) as constructor
- ▶ Parameterized by one type of fundamental gate (Atom)
 - For example, NOR or NAND
- Circuit I/O ports are defined by finite types
 - Instances of the "Fin" typeclass

Introduction

Motivation

Hardware EDSLs

Chosen EDSLs
Evaluation criteria

Modeled Circuits ALU Memory bank

Analysis of the EDSLs

ava orSyDe oquet

Coquet



Coquet: circuit example

```
Definition HADD a b s c: circuit ([:a]+[:b]) ([:s]+[:c]) :=
    Fork2 ([:a] + [:b]) |> (XOR a b s & AND a b c).
Program Definition FADD a b cin sum cout :
    circuit ([:cin] + ([:a] + [:b])) ([:sum] + [:cout]) :=
   (ONE [: cin] & HADD a b "s" "co1")
|> Rewire (* (a, (b,c)) => ((a,b), c) *)
|> (HADD cin "s" sum "co2" & ONE [: "co1"])
|> Rewire (* ((a,b), c) => (a, (b,c)) *)
|> (ONE [:sum] & OR "co2" "co1" cout).
Next Obligation. revert H; plug_def. Defined.
Next Obligation. plug_auto. Defined.
Next Obligation. revert H; plug_def. Defined.
Next Obligation. plug_auto.Defined.
```

Motivation Hardware EDSLs

Chosen EDSLs
Evaluation criteria

Modeled Circuits ALU Memory bank

Analysis of the EDSLs Lava ForSyDe Coquet



Features from the example

- Circuit I/O types (finite types)
 - Parameterized by strings: tagged units
 - Default "Fin" instances for sums, units
- Serial/Parallel composition
- Associativity plugs (reordering) automatically defined
 - With help of proof search

ALLI

Coquet





Coquet: How to prove correctness

To understand Coquet proofs, we need 2 concepts:

- Meaning relation
 - Circuit $\rightarrow Prop$
- Behavioural specification
 - What should a circuit do with its inputs

Let's take a look at the definition for each of these concepts. . .

ALLI

Coquet



Coquet: Meaning relation

```
Inductive Sem : forall {n} {m},
   C \cap m \rightarrow (n \rightarrow Data) \rightarrow (m \rightarrow Data) \rightarrow Prop :=
| KAtom: forall n m {Hfn: Fin n} {Hfm: Fin m}
           (t: techno n m) i o, spec t i o -> Sem (Atom t) i o
| KSer: forall n m p (x: C n m) (y: C m p) i mid o,
         Sem x i mid -> Sem y mid o -> Sem (Ser x y) i o
| KPar: forall n m p q (x: C n p) (y: C m q) i o,
             Sem x (select_left i) (select_left o)
         -> Sem y (select_right i) (select_right o)
         -> Sem (Par x v) i o
| KPlug: forall n m {Hfn: Fin n} {Hfm: Fin m} (f: m -> n) i,
          Sem (Plug f) i (Data.lift f i)
 KLoop: forall n m l (x: C (n + l) (m + l)) i o ret,
              Sem x (Data.app i ret) (Data.app o ret)
          -> Sem (Loop x) i o
```

Introduction

Motivation

Hardware EDSLs

Analyzed EDSLs
Chosen EDSLs
Evaluation criteria

Modeled Circuit
ALU
Memory bank
CPU

Analysis of the EDSLs Lava ForSyDe Coquet

Coquet

onclusions

Coquet: Specification

The semantics of a circuit *entails* (implies):

- ► A *relation* between inputs and outputs
- ▶ The application of a *function* to the inputs
- ▶ Up to isomorphisms...

Now for a (small) example of correctness proof...

Introduction

Motivation

Hardware EDSLs

Analyzed EDSLs
Chosen EDSLs
Evaluation criteria

Modeled Circuit ALU Memory bank

Analysis of the EDSLs Lava ForSyDe Coquet



Coquet: Correctness proofs

```
Instance HADD_Implement {a b s c}:
    Implement (HADD a b s c) _ _
        (fun (x : bool * bool) =>
            match x with (a,b) => (xorb a b, andb a b) end).
Proof.
    unfold HADD; intros ins outs H; tac.
Qed.
```

Motivation Hardware EDSLs Analyzed EDSI

Chosen EDSLs

Modeled Circuits

Memory bank CPU

Analysis of the EDSLs
Lava

Coquet

onclusions

Coquet: How to prove correctness

Hardware EDSLs
Analyzed EDSL
Chosen EDSLs
Evaluation criteri
Modeled Circui
ALU

Analysis of the EDSLs

Coquet

onclusions



boolean_eq.

Section 5

Conclusions

Introduction Motivation

Motivation Hardware EDSLs

Chosen EDSLs

Evaluation criteri

ALU Memory bank

Analysis of the EDSLs Lava

orSyDe loquet



Results

Introduction

Motivation Hardware EDSLs

Chosen EDSLs

Evaluation criteri

ALU Memory bank CPU

Analysis of the EDSLs Lava

Coquet





Future work

Motivation

ALU

Lava



Thank you!

Questions?

