

# Comparing functional Embedded Domain-Specific Languages for hardware description

João Paulo Pizani Flor

Department of Information and Computing Sciences, Utrecht University

February 13th, 2014

## Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

## Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

## Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

Lava  
ForSyDe  
Coquet

## Conclusions

Results  
Future work



Universiteit Utrecht

# Table of Contents

## Introduction

Hardware design

Domain-Specific Languages

Hardware EDSLs

## Analyzed EDSLs

Choice criteria

Chosen EDSLs

Evaluation criteria

## Modeled Circuits

Choice

ALU

Memory bank

CPU

## Analysis of the EDSLs

Lava

ForSyDe

Coquet

## Conclusions

### Introduction

Hardware design

Domain-Specific

Languages

Hardware EDSLs

### Analyzed EDSLs

Choice criteria

Chosen EDSLs

Evaluation criteria

### Modeled Circuits

Choice

ALU

Memory bank

CPU

### Analysis of the EDSLs

Lava

ForSyDe

Coquet

### Conclusions

Results

Future work



Universiteit Utrecht

# Section 1

## Introduction

### Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

### Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

### Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

### Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

### Conclusions

- Results
- Future work



# Hardware design

## Introduction

### Hardware design

- Domain-Specific Languages
- Hardware EDSLs

## Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

## Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

## Conclusions

- Results
- Future work





# Domain-Specific Languages

A computer language (turing-complete or *not*) targeting a *specific application domain*.

## Example DSLs:

- ▶ SQL (database queries)
- ▶ CSS (document formatting)
- ▶ MATLAB (Matrix programming)
- ▶ VHDL (Hardware description)

A DSL can also be *embedded* in a general-purpose language.

## Example EDSLs:

- ▶ Boost.Proto (C++ / parser combinators)
- ▶ Diagrams (Haskell / programmatic drawing)
- ▶ Parsec (Haskell / parser combinators)

### Introduction

Hardware design  
Domain-Specific  
Languages  
Hardware EDSLs

### Analyzed EDSLs

Choice criteria  
Chosen EDSLs  
Evaluation criteria

### Modeled Circuits

Choice  
ALU  
Memory bank  
CPU

### Analysis of the EDSLs

Lava  
ForSyDe  
Coquet

### Conclusions

Results  
Future work



# Example of an EDSL: Parsec

A simple parser for a "Game of Life"-like input format:

```
dead, alive :: Parser Bool
dead  = fmap (const False) (char '.')
alive = fmap (const True) (char '*')

line :: Parser [Bool]
line = many1 (dead <|> alive)

board :: Parser [[Bool]]
board = line 'endBy1' newline

parseBoardFromFile :: FilePath -> IO [[Bool]]
parseBoardFromFile filename = do
  result <- parseFromFile board filename
  return $ either (error . show) id result
```

## Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

## Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

## Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

## Conclusions

- Results
- Future work



## Hardware EDSLs

An EDSL used for hardware design-related tasks. Can encompass:

- ▶ Modelling / description
- ▶ Simulation (validation)
- ▶ Formal verification
- ▶ Synthesis to other (lower-level) languages

## Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

## Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

## Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

Lava  
ForSyDe  
Coquet

## Conclusions

Results

Future work





# Example of a hardware EDSL

Some Lava code. . .

## Introduction

- Hardware design
- Domain-Specific Languages

## Hardware EDSLs

## Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

## Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

## Conclusions

- Results
- Future work



# Section 2

## Analyzed EDSLs

### Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

### Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

### Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

### Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

### Conclusions

- Results
- Future work



# Choice criteria

## Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

## Analyzed EDSLs

### Choice criteria

- Chosen EDSLs
- Evaluation criteria

## Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

## Conclusions

- Results
- Future work



# Chosen EDSLs

The language we chose to evaluate, with the respective host language, were:

- ▶ Lava (Haskell - *chalmers-lava dialect*)
- ▶ ForSyDe (Haskell)
- ▶ Coquet (Coq interactive theorem prover)

## Introduction

Hardware design  
Domain-Specific  
Languages  
Hardware EDSLs

## Analyzed EDSLs

Choice criteria  
**Chosen EDSLs**  
Evaluation criteria

## Modeled Circuits

Choice  
ALU  
Memory bank  
CPU

## Analysis of the EDSLs

Lava  
ForSyDe  
Coquet

## Conclusions

Results  
Future work



## Evaluation criteria

- ▶ Simulation
- ▶ Verification
- ▶ Genericity
- ▶ Depth of embedding
- ▶ Tool integration
- ▶ Extensibility

## Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

## Analyzed EDSLs

Choice criteria  
Chosen EDSLs

### Evaluation criteria

## Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

Lava  
ForSyDe  
Coquet

## Conclusions

Results  
Future work



# Section 3

## Modeled Circuits

### Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

### Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

### Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

### Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

### Conclusions


- Results
- Future work





# Chosen circuits

We cherry-picked circuits from the book “Elements of Computing Systems”, as they satisfied all of our demands.

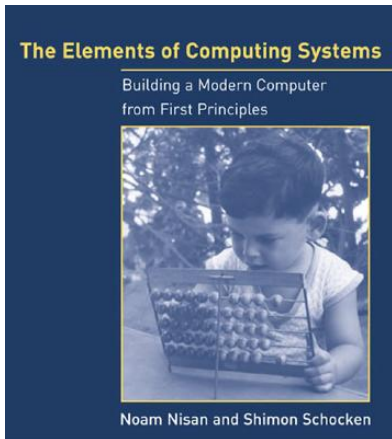

**Figure:** “Elements of Computing Systems” - Nisan, Schocken, available at <http://www.nand2tetris.org>.

## Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

## Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

## Modeled Circuits

### Choice

- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

## Conclusions

- Results
- Future work



Universiteit Utrecht



# Chosen circuits

**Circuit 1** A 2-input, 16-bit-wide, simple ALU

**Circuit 2** A 64-word long, 16-bit wide memory block

**Circuit 3** An *extremely* reduced instruction set CPU, the *Hack* CPU.

Let's take a quick look at each of these circuit's specification. . .

## Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

## Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

## Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet


## Conclusions

- Results
- Future work





# Circuit 1: block diagram

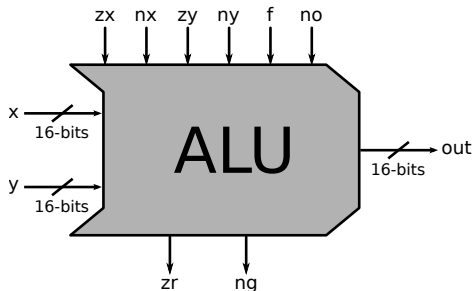

**Figure:** Input/Output ports of *circuit 1*, the ALU.

## Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

## Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

## Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

## Conclusions

- Results
- Future work



Universiteit Utrecht

# Circuit 1: specification

The behaviour of the ALU is specified by the values of the *control bits* and *flags*:

**zx and zy** Zeroes the “x” and “y” inputs, respectively

**nx and ny** *bitwise negation* on the “x” and “y” inputs

**f** Selects the function to be applied:

“f” = 1 for addition, “f” = 0 for bitwise AND

**no** *bitwise negation* on the output ALU output

**zr and ng** The output *flag* “zr” = 1 *iff* the ALU output is zero. “ng” = 1 *iff* the output is negative.

Formal definition and test cases in the book.

## Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

## Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

## Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

## Conclusions

- Results
- Future work



# Circuit 2: RAM64

Some of the circuit's key characteristics:

- ▶ *Sequential* circuit, with clock input
- ▶ 64 memory words stored, each 16-bit wide
- ▶ Address port has width  $\log_2 64 = 6$  bit

## Introduction

Hardware design  
Domain-Specific  
Languages  
Hardware EDSLs

## Analyzed EDSLs

Choice criteria  
Chosen EDSLs  
Evaluation criteria

## Modeled Circuits

Choice  
ALU  
Memory bank  
CPU

## Analysis of the EDSLs


Lava  
ForSyDe  
Coquet

## Conclusions

Results  
Future work



## Circuit 2: block diagram

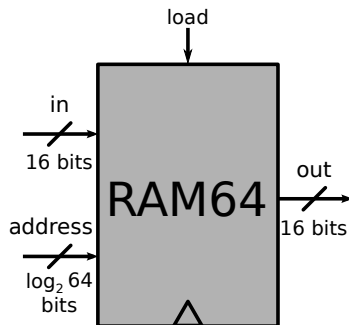

**Figure:** Input/Output ports of *circuit 2*, the RAM64 block.

### Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

### Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

### Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

### Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

### Conclusions

- Results
- Future work



# Circuit 2: specification

- ▶ The output “out” holds the value at the memory line indicated by “address”.
- ▶ *Iff* “load” = 1, then the value at input “in” will be loaded into memory line “address”.
- ▶ The loaded value will be emitted on “out” at the *next* clock cycle.

## Introduction

Hardware design  
Domain-Specific  
Languages  
Hardware EDSLs

## Analyzed EDSLs

Choice criteria  
Chosen EDSLs  
Evaluation criteria

## Modeled Circuits

Choice  
ALU  
Memory bank  
CPU

## Analysis of the EDSLs

Lava  
ForSyDe  
Coquet

## Conclusions


Results  
Future work







## Circuit 3: block diagram

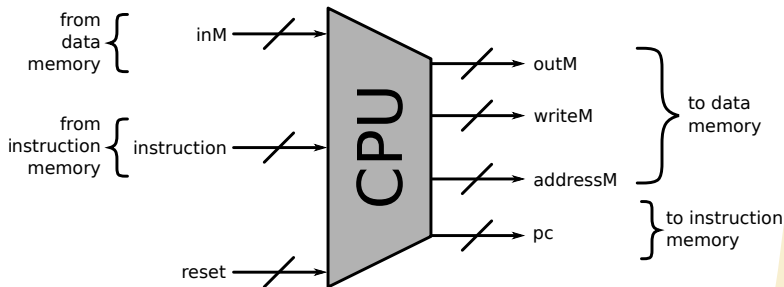

**Figure:** Input/Output ports of *circuit 3*, the *Hack CPU*.

### Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

### Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

### Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

### Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

### Conclusions


- Results
- Future work


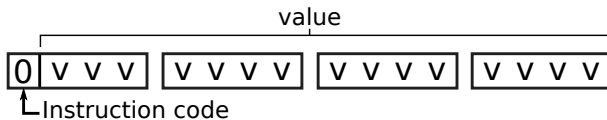
# Circuit 3: specification

Circuit 3 runs “A” and “C” instructions, according to the *Hack assembly specification*.

- ▶ The “A” instruction: sets the “A” register.



- ▶ The value in “A” can be used:
  - As operand for a subsequent computation
  - As address for jumps

## Introduction

Hardware design  
Domain-Specific  
Languages  
Hardware EDSLs

## Analyzed EDSLs

Choice criteria  
Chosen EDSLs  
Evaluation criteria

## Modeled Circuits

Choice  
ALU  
Memory bank  
CPU

## Analysis of the EDSLs

Lava  
ForSyDe  
Coquet

## Conclusions

Results  
Future work




Universiteit Utrecht
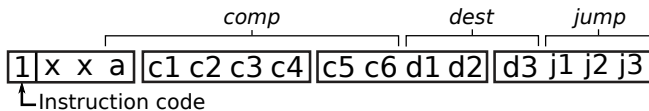
# Circuit 3: specification

Circuit 3 runs “A” and “C” instructions, according to the *Hack assembly specification*.

- ▶ The “C” instruction: sets the “C” register, performs *computation* or jumps.



- ▶ Some peculiarities:
  - Bits “c1” to “c6” control the ALU
  - *conditional* or *unconditional* jumps
  - *destination* of the computation result: “A”, “D”, “M”

## Introduction

Hardware design  
Domain-Specific  
Languages  
Hardware EDSLs

## Analyzed EDSLs

Choice criteria  
Chosen EDSLs  
Evaluation criteria

## Modeled Circuits

Choice  
ALU  
Memory bank  
CPU

## Analysis of the EDSLs


Lava  
ForSyDe  
Coquet

## Conclusions

Results  
Future work



# Circuit 3: specification (parts)

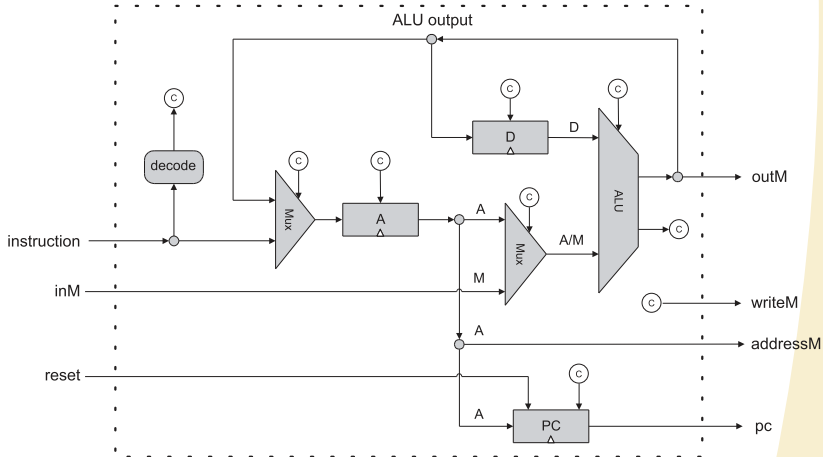

**Figure:** Parts used to build the *Hack* CPU, and their interconnection.

## Introduction

Hardware design  
Domain-Specific  
Languages  
Hardware EDSLs

## Analyzed EDSLs

Choice criteria  
Chosen EDSLs  
Evaluation criteria

## Modeled Circuits

Choice  
ALU  
Memory bank  
CPU

## Analysis of the EDSLs

Lava  
ForSyDe  
Coquet

## Conclusions

Results  
Future work



# Section 4

## Analysis of the EDSLs

### Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

### Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

### Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

### Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

### Conclusions

- Results
- Future work



# Lava: Adders

```
type SB = Signal Bool

halfAdder :: (SB, SB) -> (SB, SB)
halfAdder inputs = (xor2 inputs, and2 inputs)

fullAdder :: (SB, (SB, SB)) -> (SB, SB)
fullAdder (cin, (a, b)) = (s, cout)
  where
    (ab, c1) = halfAdder (a, b)
    (s, c2)  = halfAdder (ab, cin)
    cout    = or2 (c1, c2)

rippleCarryAdder :: [(SB, SB)] -> [SB]
rippleCarryAdder ab = s
  where (s, _) = row fullAdder (low, ab)
```

## Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

## Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

## Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

## Conclusions

- Results
- Future work





# Lava: ALU

```
type ALUControlBits = (SB, SB, SB, SB, SB, SB)

alu :: ([SB], [SB], ALUControlBits) -> ([SB], SB, SB)
alu (x, y, (zx, nx, zy, ny, f, no)) = (out', zr, ng)
  where x'      = mux (zx, (x, replicate (length x) low))
        x''     = mux (nx, (x', map inv x'))
        y'      = mux (zy, (y, replicate (length x) low))
        y''     = mux (ny, (y', map inv y'))
        out     = let xy'' = zip x'' y''
                  in mux (f, (and1 xy'', adder xy''))
        out'    = mux (no, (out, map inv out))
        zr      = foldl (curry and2) low out'
        ng      = equalBool high (last out')
        adder   = rippleCarryAdder
```

## Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

## Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

## Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

## Conclusions

- Results
- Future work





## Remarks

- ▶ Cannot introduce new, meaningful datatypes
  - Only Signal Bool is synthesizable
  - Or tuples/lists thereof
- ▶ Input/Output types have to be *uncurried*
- ▶ Weak type-safety over the inputs/outputs
  - Working with tuples is tiresome and has limitations
  - Lists don't enforce *size* constraints

## Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

## Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

## Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

Lava  
ForSyDe  
Coquet

## Conclusions

Results

Future work



# Lava: RAM64

```
reg :: (SB, SB) -> SB
reg (input, load) = out
  where dff = mux (load, (out, input))
        out = delay low dff

regN :: Int -> ([SB], SB) -> [SB]
regN n (input, load) = map reg $ zip input (replicate n load)

ram64Rows :: Int -> ([SB], (SB,SB,SB,SB,SB,SB,SB), SB) -> [SB]
ram64Rows n (input, addr, load) = mux64WordN n (addr, regs)
  where memLine sel = regN n (input, sel <&> load)
        regs        = map memLine (decode6To64 addr)
```

## Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

## Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

## Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

## Conclusions

- Results
- Future work



## Remarks

Positive:

- ▶ Uses host language for binding (let/where) and recursion
- ▶ Uses host language for structural combinators

Negative:

- ▶ Again, weak type-safety of lists, can cause problems at simulation
- ▶ *No modularity* in the generated VHDL code.

## Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

### Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

## Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

Lava  
ForSyDe  
Coquet

## Conclusions

Results

Future work



Universiteit Utrecht

# Lava: *Hack* CPU

## Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

## Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

## Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

### Lava

- ForSyDe
- Coquet

## Conclusions

- Results
- Future work



## Remarks

Could benefit from:

- ▶ Fixed-length vectors
  - ForSyDe-style or with type-level naturals in recent GHC.

## Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

## Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

## Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

Lava  
ForSyDe  
Coquet

## Conclusions

- Results
- Future work



# ForSyDe: ALU (non-synth)

```
type S = Signal
type Word = Int16

data ALUOp = ALUSum | ALUAnd
    deriving (Typeable, Data, Show)

$(deriveLift1 ''ALUOp)

type ALUCtrl = (Bit, Bit, Bit, Bit, ALUOp, Bit)
type ALUFlag = (Bit, Bit)

bo, bb :: Bit -> Bool
bo = bitToBool
bb = boolToBit
```

## Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

## Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

## Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

## Conclusions

- Results
- Future work



# ForSyDe: ALU (non-synth)

```
aluFunc :: ProcFunc (ALUCtrl -> Word -> Word -> (Word,ALUFlag))
aluFunc = $(newProcFun [d|
  aluFunc' (zx,nx,zy,ny,f,no) x y =
    ( out,  (bb (out == 0), bb (out < 0)) )
  where
    zf z w  = if bo z then 0 else w
    nf n w  = if bo n then complement w else w
    (xn, yn) = (nf nx $ zf zx $ x,  nf ny $ zf zy $ y)
    out      = nf no $ case f of
                        ALUSum -> xn + yn
                        ALUAnd -> xn .&. yn  |] )

aluProc :: S ALUCtrl -> S Word -> S Word -> S (Word,ALUFlag)
aluProc = zipWith3SY "aluProc" aluFunc
```

## Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

## Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

## Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

## Conclusions

- Results
- Future work



# ForSyDe: Muxes

```
mux2 :: S Bit -> S Word -> S Word -> S Word
mux2 = zipWith3SY "zipWith3SY" $(newProcFun [d]
  f s x y = if s == L then x else y [])
```

```
mux2SysDef :: SysDef (S Bit -> S Word -> S Word -> S Word)
mux2SysDef = newSysDef mux2 "mux2" ["s","i1","i2"] ["o"]
```

```
mux4 :: S (FSVec D2 Bit) -> S (FSVec D4 Word) -> S Word
mux4 ss is = (mux2' "m1") (sv ! d1) m00 m01 where
  mux2' l = instantiate l mux2SysDef
  sv      = unzipxSY "unzipSel" ss
  iv      = unzipxSY "unzipInp" is
  m00     = (mux2' "m00") (sv ! d0) (iv ! d0) (iv ! d1)
  m01     = (mux2' "m01") (sv ! d0) (iv ! d2) (iv ! d3)
```

```
mux4SysDef :: SysDef ( S (FSVec D2 Bit) -> S (FSVec D4 Word)
                      -> S Word)
mux4SysDef = newSysDef mux4 "mux4" ["s","is"] ["o"]
```

## Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

## Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

## Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

## Conclusions

- Results
- Future work



Universiteit Utrecht



# ForSyDe: RAM64

```
reg :: S Word -> S Bit -> S Word
reg input load = out where
  out = delaySY "delay" (0 :: WordType) dff
  dff = (instantiate "mux2" mux2SysDef) load out input

ram64 :: S Word -> S (FVec D6 Bit) -> S Bit -> S Word
ram64 input addr load = mux' addr (zipxSY "zipRows" rs) where
  mux'      = instantiate "mux" mux64SysDef
  decoder'  = instantiate "decoder" decode6To64SysDef
  reg' l    = instantiate l regSysDef
  and' l    = instantiate l andSysDef
  r (s,l)   = (reg' l) input ((and' (l ++ ":and")) load s)
  rs'       = unzipxSY "unzipAddr" $ decoder' addr
  rs        = V.map r $ V.zip rs' (V.map (\n -> "r" ++ show n)
                                     (V.unsafeVector d64 [0..63]))

ram64SysDef = newSysDef ram64 "ram64" ["i","a","l"] ["o"]
```

## Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

## Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

## Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

## Conclusions

- Results
- Future work



Universiteit Utrecht

# The Circuit type

```
Context {tech : Techno}
Inductive Circuit : Type -> Type -> Type :=
| Atom : forall {n m : Type} {Hfn : Fin n} {Hfm : Fin m},
        techno n m -> Circuit n m

| Plug : forall {n m : Type} {Hfn : Fin n} {Hfm : Fin m}
        (f : m -> n), Circuit n m

| Ser : forall {n m p : Type},
        Circuit n m -> Circuit m p -> Circuit n p

| Par : forall {n m p q : Type},
        Circuit n p -> Circuit m q
        -> Circuit (n + m) (p + q)

| Loop : forall {n m p : Type},
        Circuit (n + p) (n + p) -> Circuit n m
```

## Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

## Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

## Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

## Conclusions

- Results
- Future work



# Coquet

```
Definition HADD a b s c: circuit ([:a] + [:b]) ([:s] + [:c]) :=  
  Fork2 ([:a] + [:b])  
  |> (XOR a b s & AND a b c).
```

## Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

## Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

## Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet**

## Conclusions

- Results
- Future work



```
Program Definition FADD a b cin sum cout :  
  circuit ([:cin] + ([:a] + [:b])) ([:sum] + [:cout]) :=  
  
    (ONE [: cin] & HADD a b "s" "co1")  
|> Rewire (* (a, (b,c)) => ((a,b), c) *)  
|> (HADD cin "s" sum "co2" & ONE [: "co1"])  
|> Rewire (* ((a,b), c) => (a, (b,c)) *)  
|> (ONE [:sum] & OR "co2" "co1" cout).
```

Next Obligation. revert H; plug\_def. Defined.

Next Obligation. plug\_auto. Defined.

Next Obligation. revert H; plug\_def. Defined.

Next Obligation. plug\_auto. Defined.

## Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

## Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

## Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

## Conclusions

- Results
- Future work



# Coquet: Meaning relation

```
Inductive Sem : forall {n} {m},  
  C n m -> (n -> Data) -> (m -> Data) -> Prop :=  
  
| KAtom: forall n m {Hfn: Fin n} {Hfm: Fin m}  
  (t: techno n m) i o, spec t i o -> Sem (Atom t) i o  
  
| KSer: forall n m p (x: C n m) (y: C m p) i mid o,  
  Sem x i mid -> Sem y mid o -> Sem (Ser x y) i o  
  
| KPar: forall n m p q (x: C n p) (y: C m q) i o,  
  Sem x (select_left i) (select_left o)  
  -> Sem y (select_right i) (select_right o)  
  -> Sem (Par x y) i o  
  
| KPlug: forall n m {Hfn: Fin n} {Hfm: Fin m} (f: m -> n) i,  
  Sem (Plug f) i (Data.lift f i)  
  
| KLoop: forall n m l (x: C (n + l) (m + l)) i o ret,  
  Sem x (Data.app i ret) (Data.app o ret)  
  -> Sem (Loop x) i o
```

## Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

## Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

## Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

## Conclusions

- Results
- Future work



Universiteit Utrecht

# Coquet: Specification

```
Context {n m N M : Type}
  (Rn : Iso (n -> T) N) (Rm : Iso (m -> T) M).

Class Realise (c : Circuit n m) (R : N -> M -> Prop) :=
  realise: forall i o, Semantics c i o -> R (iso i) (iso o)

Class Implement (c : Circuit n m) (f : N -> M) :=
  implement: forall i o, Semantics c i o -> iso o = f (iso i)
```

## Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

## Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

## Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

## Conclusions

- Results
- Future work



# Coquet: Correctness proofs

```
Instance HADD_Implement {a b s c} :  
  Implement (HADD a b s c) _ _  
  (fun (x : bool * bool) =>  
    match x with (a,b) => (xorb a b, andb a b) end).  
Proof.  
  unfold HADD; intros ins outs H; tac.  
Qed.
```

## Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

## Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

## Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet**

## Conclusions

- Results
- Future work



# Coquet: How to prove correctness

```
Ltac tac :=  
  rinvert; (* destruct the circuit *)  
  realise_all; (* use the hint data-base *)  
  unreify_all bool; (* unreify *)  
  destruct_all; (* destruct the booleans *)  
  intros_all;  
  clear;  
  boolean_eq.
```

## Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

## Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

## Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet**

## Conclusions

- Results
- Future work





# Section 5

## Conclusions

### Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

### Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

### Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

### Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

### Conclusions

- Results
- Future work



# Results

## Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

## Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

## Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

## Conclusions

- Results**
- Future work



# Future work

## Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

## Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

## Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

## Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

## Conclusions

- Results
- Future work



Thank you!

Questions?

