

Comparing functional Embedded Domain-Specific Languages for hardware description

João Paulo Pizani Flor

Department of Information and Computing Sciences, Utrecht University

February 13th, 2014

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

Lava
ForSyDe
Coquet

Conclusions



Universiteit Utrecht

Table of Contents

Introduction

Hardware design

Domain-Specific Languages

Hardware EDSLs

Analyzed EDSLs

Choice criteria

Chosen EDSLs

Evaluation criteria

Modeled Circuits

Choice

ALU

Memory bank

CPU

Analysis of the EDSLs

Lava

ForSyDe

Coquet

Conclusions

Introduction

Hardware design

Domain-Specific
Languages

Hardware EDSLs

Analyzed EDSLs

Choice criteria

Chosen EDSLs

Evaluation criteria

Modeled Circuits

Choice

ALU

Memory bank

CPU

Analysis of the EDSLs

Lava

ForSyDe

Coquet

Conclusions



Section 1

Introduction

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



Hardware design

Introduction

Hardware design

- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



Domain-Specific Languages

A computer language (turing-complete or *not*) targeting a *specific application domain*.

Example DSLs:

- ▶ SQL (database queries)
- ▶ CSS (document formatting)
- ▶ MATLAB (Matrix programming)
- ▶ VHDL (Hardware description)

A DSL can also be *embedded* in a general-purpose language.

Example EDSLs:

- ▶ Boost.Proto (C++ / parser combinators)
- ▶ Diagrams (Haskell / programmatic drawing)
- ▶ Parsec (Haskell / parser combinators)

Introduction

Hardware design
Domain-Specific
Languages
Hardware EDSLs

Analyzed EDSLs

Choice criteria
Chosen EDSLs
Evaluation criteria

Modeled Circuits

Choice
ALU
Memory bank
CPU

Analysis of the EDSLs

Lava
ForSyDe
Coquet

Conclusions



Example of an EDSL: Parsec

A simple parser for a "Game of Life"-like input format:

```
dead, alive :: Parser Bool
dead  = fmap (const False) (char '.')
alive = fmap (const True)  (char '*')

line :: Parser [Bool]
line  = many1 (dead <|> alive)

board :: Parser [[Bool]]
board = line 'endBy1' newline

parseBoardFromFile :: FilePath -> IO [[Bool]]
parseBoardFromFile filename = do
  result <- parseFromFile board filename
  return $ either (error . show) id result
```

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



Hardware EDSLs

An EDSL used for hardware design-related tasks. Can encompass:

- ▶ Modeling / description
- ▶ Simulation (validation)
- ▶ Formal verification
- ▶ Synthesis to other (lower-level) languages

Introduction

Hardware design
Domain-Specific
Languages
Hardware EDSLs

Analyzed EDSLs

Choice criteria
Chosen EDSLs
Evaluation criteria

Modeled Circuits

Choice
ALU
Memory bank
CPU

Analysis of the EDSLs

Lava
ForSyDe
Coquet

Conclusions



Example of a hardware EDSL

Some Lava code. . .

Introduction

- Hardware design
- Domain-Specific Languages

Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



Section 2

Analyzed EDSLs

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



Choice criteria

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

Choice criteria

- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



Chosen EDSLs

The language we chose to evaluate, with the respective host language, were:

- ▶ Lava (Haskell - *chalmers-lava dialect*)
- ▶ ForSyDe (Haskell)
- ▶ Coquet (Coq interactive theorem prover)

Introduction

Hardware design
Domain-Specific
Languages
Hardware EDSLs

Analyzed EDSLs

Choice criteria
Chosen EDSLs
Evaluation criteria

Modeled Circuits

Choice
ALU
Memory bank
CPU

Analysis of the EDSLs

Lava
ForSyDe
Coquet

Conclusions



Section 3

Modeled Circuits

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



Chosen circuits

We cherry-picked circuits from the book “Elements of Computing Systems”, as they satisfied all of our demands.

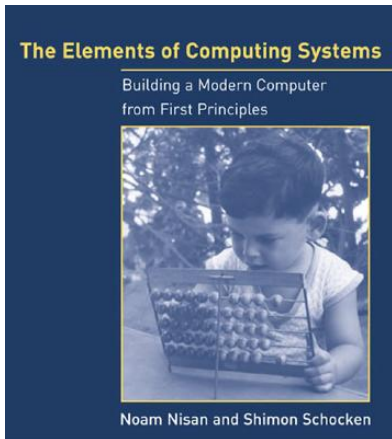


Figure: “Elements of Computing Systems” - Nisan, Schocken, available at <http://www.nand2tetris.org>.

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

Choice

- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



Universiteit Utrecht

Chosen circuits

Circuit 1 A 2-input, 16-bit-wide, simple ALU

Circuit 2 A 64-word long, 16-bit wide memory block

Circuit 3 An *extremely* reduced instruction set CPU, the *Hack* CPU.

Let's take a quick look at each of these circuit's specification. . .

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



Circuit 1: ALU

Some of the circuit's key characteristics:

- ▶ 2 operand inputs and 1 operand output, each 16-bit wide
- ▶ 1 output flag
- ▶ Can execute 18 different *functions*, among which:
 - Addition, subtraction
 - Bitwise AND / OR
 - Constant outputs
 - Addition of constants to an operand
 - Sign inversion

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

Choice
ALU
Memory bank
CPU

Analysis of the EDSLs

Lava
ForSyDe
Coquet

Conclusions



Circuit 1: block diagram

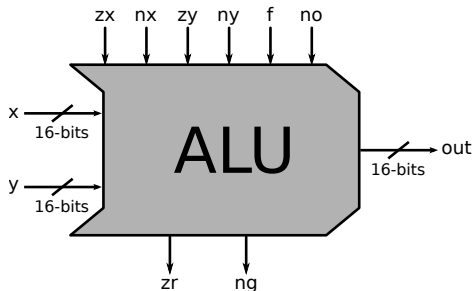


Figure: Input/Output ports of *circuit 1*, the ALU.

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



Circuit 1: specification

The behaviour of the ALU is specified by the values of the *control bits* and *flags*:

zx and zy Zeroes the “x” and “y” inputs, respectively

nx and ny *bitwise negation* on the “x” and “y” inputs

f Selects the function to be applied:

“f” = 1 for addition, “f” = 0 for bitwise AND

no *bitwise negation* on the output ALU output

zr and ng The output *flag* “zr” = 1 *iff* the ALU output is zero. “ng” = 1 *iff* the output is negative.

Formal definition and test cases in the book.

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



Circuit 2: RAM64

Some of the circuit's key characteristics:

- ▶ *Sequential* circuit, with clock input
- ▶ 64 memory words stored, each 16-bit wide
- ▶ Address port has width $\log_2 64 = 6$ bit

Introduction

Hardware design
Domain-Specific
Languages
Hardware EDSLs

Analyzed EDSLs

Choice criteria
Chosen EDSLs
Evaluation criteria

Modeled Circuits

Choice
ALU
Memory bank
CPU

Analysis of the EDSLs

Lava
ForSyDe
Coquet

Conclusions



Circuit 2: block diagram

 


Figure: Input/Output ports of *circuit 2*, the RAM64 block.

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



Circuit 2: specification

- ▶ The output “out” holds the value at the memory line indicated by “address”.
- ▶ *Iff* “load” = 1, then the value at input “in” will be loaded into memory line “address”.
- ▶ The loaded value will be emitted on “out” at the *next* clock cycle.

Introduction

Hardware design
Domain-Specific
Languages
Hardware EDSLs

Analyzed EDSLs

Choice criteria
Chosen EDSLs
Evaluation criteria

Modeled Circuits

Choice
ALU
Memory bank
CPU

Analysis of the EDSLs

Lava
ForSyDe
Coquet

Conclusions



Circuit 3: block diagram

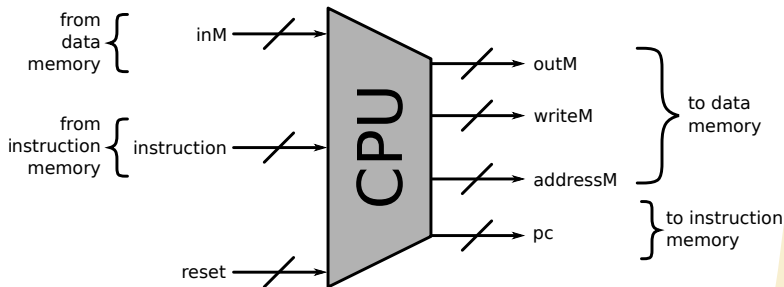


Figure: Input/Output ports of *circuit 3*, the *Hack CPU*.

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet


Conclusions



Circuit 3: specification

Circuit 3 runs “A” and “C” instructions, according to the *Hack assembly specification*.

 - ▶ The “A” instruction: sets the “A” register.



- ▶ The value in “A” can be used:
 - As operand for a subsequent computation
 - As address for jumps

Introduction

Hardware design
Domain-Specific
Languages
Hardware EDSLs

Analyzed EDSLs

Choice criteria
Chosen EDSLs
Evaluation criteria

Modeled Circuits

Choice
ALU
Memory bank
CPU

Analysis of the EDSLs

Lava
ForSyDe
Coquet

Conclusions




Universiteit Utrecht

Circuit 3: specification

Circuit 3 runs “A” and “C” instructions, according to the *Hack assembly specification*.

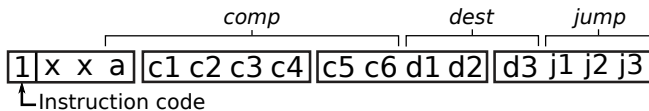- ▶ The “C” instruction: sets the “C” register, performs *computation* or jumps.



- ▶ Some peculiarities:
 - Bits “c1” to “c6” control the ALU
 - *conditional* or *unconditional* jumps
 - *destination* of the computation result: “A”, “D”, “M”

Introduction

Hardware design
Domain-Specific
Languages
Hardware EDSLs

Analyzed EDSLs

Choice criteria
Chosen EDSLs
Evaluation criteria

Modeled Circuits

Choice
ALU
Memory bank
CPU

Analysis of the EDSLs

Lava
ForSyDe
Coquet

Conclusions



Universiteit Utrecht

Circuit 3: specification (parts)

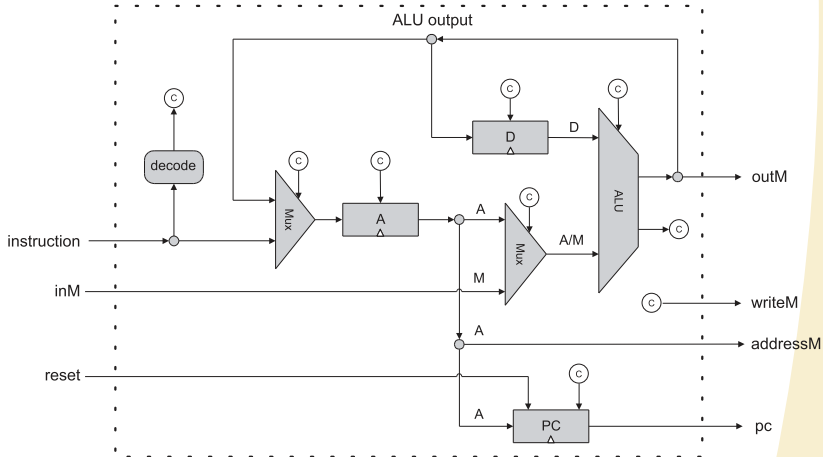


Figure: Parts used to build the *Hack* CPU, and their interconnection.

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



Section 4

Analysis of the EDSLs

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



Lava

- ▶ Developed at Chalmers University of Technology, Sweden
 - Initially by Koen Claessen and Mary Sheeran
 - Later also Per Bjesse and David Sands
- ▶ Has several *dialects*
 - chalmers-lava, xilinx-lava, kansas-lava, etc.
 - We focus on the “canonical” chalmers-lava

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

Lava
ForSyDe
Coquet

Conclusions



Universiteit Utrecht

Lava: Adders

```
type SB = Signal Bool

halfAdder :: (SB, SB) -> (SB, SB)
halfAdder inputs = (xor2 inputs, and2 inputs)

fullAdder :: (SB, (SB, SB)) -> (SB, SB)
fullAdder (cin, (a, b)) = (s, cout)
  where
    (ab, c1) = halfAdder (a, b)
    (s, c2)  = halfAdder (ab, cin)
    cout    = or2 (c1, c2)

rippleCarryAdder :: [(SB, SB)] -> [SB]
rippleCarryAdder ab = s
  where (s, _) = row fullAdder (low, ab)
```

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



Lava: Simulation and verification

► A taste of simulation in Lava:

```
type SB = Signal Bool
testHalfAdder :: [(SB, SB)]
testHalfAdder = map (simulate halfAdder) input
  where input = [ (low,low), (low,high)
                  , (high,low), (high,high)]
```

- Cannot be easily automated: equality of Signal is non-trivial

► And verification...

```
prop_FullAdderCommutative :: (SB, (SB, SB)) -> SB
prop_FullAdderCommutative (c, (a, b)) =
  fullAdder (c, (a, b)) <==> fullAdder (c, (b, a))

-- satzoo prop_FullAdderCommutative
```

- Advantage: Used in conjunction with an external SAT solver (e.g. *Satzoo*)
- Disadvantage: Only verifies instances of *specific size*

Introduction

Hardware design
Domain-Specific
Languages
Hardware EDSLs

Analyzed EDSLs

Choice criteria
Chosen EDSLs
Evaluation criteria

Modeled Circuits

Choice
ALU
Memory bank
CPU

Analysis of the EDSLs

Lava
ForSyDe
Coquet

Conclusions



Lava: ALU

```
type ALUControlBits = (SB, SB, SB, SB, SB, SB)

alu :: ([SB], [SB], ALUControlBits) -> ([SB], SB, SB)
alu (x, y, (zx, nx, zy, ny, f, no)) = (out', zr, ng)
  where x'      = mux (zx, (x, replicate (length x) low))
        x''     = mux (nx, (x', map inv x'))
        y'      = mux (zy, (y, replicate (length x) low))
        y''     = mux (ny, (y', map inv y'))
        out     = let xy'' = zip x'' y''
                  in mux (f, (and1 xy'', adder xy''))
        out'    = mux (no, (out, map inv out))
        zr      = foldl (curry and2) low out'
        ng      = equalBool high (last out')
        adder   = rippleCarryAdder
```

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



Remarks

- ▶ Cannot introduce new, meaningful datatypes
 - Only Signal Bool is synthesizable
 - Or tuples/lists thereof
- ▶ Input/Output types have to be *uncurried*
- ▶ Weak type-safety over the inputs/outputs
 - Working with tuples is tiresome and has limitations
 - Lists don't enforce size constraints

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

Lava
ForSyDe
Coquet

Conclusions



Lava: RAM64

```
reg :: (SB, SB) -> SB
reg (input, load) = out
  where dff = mux (load, (out, input))
        out = delay low dff

regN :: Int -> ([SB], SB) -> [SB]
regN n (input, load) = map reg $ zip input (replicate n load)

ram64Rows :: Int -> ([SB], (SB,SB,SB,SB,SB,SB,SB), SB) -> [SB]
ram64Rows n (input, addr, load) = mux64WordN n (addr, regs)
  where memLine sel = regN n (input, sel <&> load)
        regs         = map memLine (decode6To64 addr)
```

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



Remarks

Positive:

- ▶ Uses host language for binding (let/where) and recursion
- ▶ Uses host language for structural combinators

Negative:

- ▶ Again, weak type-safety of lists
 - Extra Int parameter controls port sizes
- ▶ *No modularity* in the generated VHDL code.

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

Lava
ForSyDe
Coquet

Conclusions



Universiteit Utrecht

Lava: *Hack* CPU (some parts)

```
programCounter :: Int -> (SB, SB, [SB]) -> [SB]
programCounter n (reset, set, input) = out where
    incr      = increment out
    out       = delay (replicate n low) increset
    incinput  = mux (set, (incr, input))
    increset  = mux (reset, (incinput, replicate n low))

type Dest      = (SB, SB, SB)
type JumpCond  = (SB, SB, SB)
type CPUCtrl   = (SB, SB, Dest, JumpCond, ALUCtrl)

instructionDecoder :: HackInstruction -> CPUCtrl
instructionDecoder (i0,_,_,i3,i4,i5,i6,i7,i8,i9,...,i15)
    = (aFlag, cAM, cDest, cJump, cALU) where
    aFlag = i0
    cAM   = inv i3
    cDest = (i10, i11, i12)
    cJump = (i13, i14, i15)
    cALU  = (i4, i5, i6, i7, i8, i9)
```

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



Remarks

Could benefit from:

- ▶ Fixed-length vectors
 - ForSyDe-style or with type-level naturals in recent GHC.
- ▶ Slicing operators over vectors
- ▶ *Synthesizable* user-defined datatypes

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

Lava
ForSyDe
Coquet

Conclusions



- ▶ Based on the “Formal System Design” approach
 - Royal Institute of Technology - KTH, Sweden
- ▶ Available for Haskell and SystemC
- ▶ Has BOTH shallow and deep-embedded “versions”
 - Same library, subtle distinction
 - Will become clearer with examples
- ▶ *Template Haskell* to express circuits with Haskell syntax

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

Lava
ForSyDe
Coquet

Conclusions



ForSyDe's key concepts

- ▶ Models of Computation (MoCs)
 - We focus on the *synchronous* MoC
- ▶ Processes
 - A process belongs to a MoC
 - Built with a *process constructor*
- ▶ Signals
 - Connections among processes

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU


Analysis of the EDSLs

Lava
ForSyDe
Coquet

Conclusions



ForSyDe's key concepts

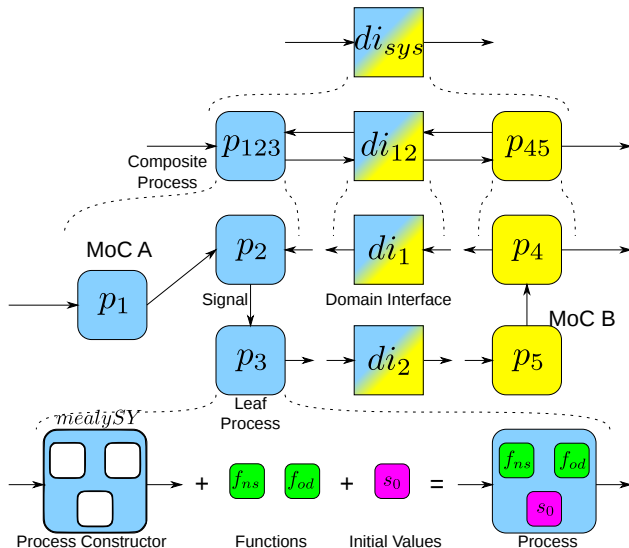

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

Lava
ForSyDe
Coquet

Conclusions



Universiteit Utrecht

ForSyDe: ALU (non-synth)

```
type S = Signal
type Word = Int16

data ALUOp = ALUSum | ALUAnd
  deriving (Typeable, Data, Show)

$(deriveLift1 ''ALUOp)

type ALUCtrl = (Bit, Bit, Bit, Bit, ALUOp, Bit)
type ALUFlag = (Bit, Bit)

bo, bb :: Bit -> Bool
bo = bitToBool
bb = boolToBit
```

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



ForSyDe: ALU (non-synth)

```
aluFunc :: ProcFunc (ALUCtrl -> Word -> Word -> (Word,ALUFlag))
aluFunc = $(newProcFun [d|
  aluFunc' (zx,nx,zy,ny,f,no) x y =
    ( out,  (bb (out == 0), bb (out < 0)) )
  where
    zf z w  = if bo z then 0 else w
    nf n w  = if bo n then complement w else w
    (xn, yn) = (nf nx $ zf zx $ x,  nf ny $ zf zy $ y)
    out      = nf no $ case f of
                        ALUSum -> xn + yn
                        ALUAnd -> xn .&. yn  |] )

aluProc :: S ALUCtrl -> S Word -> S Word -> S (Word,ALUFlag)
aluProc = zipWith3SY "aluProc" aluFunc
```

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



Universiteit Utrecht

ForSyDe: synthesis restrictions

Restrictions imposed on a model by ForSyDe so that it can be translated to VHDL:

- ▶ ProcFun-related:
 - Limited argument types (instances of ProcType)
 - Int, Int8, ..., Bool, Bit
 - Enumerated types (deriving Data and Lift)
 - Tuples and FSVec's
- ▶ VHDL engine-related:
 - No point-free notation
 - Single clause / no pattern matching
 - No where or let bindings

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

Lava
ForSyDe
Coquet

Conclusions



ForSyDe: ALU (synthesizable)

```
zProc :: ProcId -> S Bit -> S Word -> S Word
```

```
zProc name = zipWithSY name $(newProcFun [d|
```

```
  f :: Bit -> Word -> Word
```

```
  f z w = if z == H then 0 else w |])
```

```
nProc :: ProcId -> S Bit -> S Word -> S Word
```

```
nProc name = zipWithSY name $(newProcFun [d|
```

```
  f :: Bit -> Word -> Word
```

```
  f n w = if n == H then negate w else w |])
```

```
compProc :: S Bit -> S Word -> S Word -> S Word
```

```
compProc = zipWith3SY "compProc" $(newProcFun [d|
```

```
  f :: Bit -> Word -> Word -> Word
```

```
  f o x y = if o == H then x + y else x .&. y |])
```

```
tzProc :: S Word -> S Bit ...
```

```
tnProc :: S Word -> S Bit ...
```

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



Universiteit Utrecht

ForSyDe: ALU (synthesizable)

```
type ALUCtrl = (Bit, Bit, Bit, Bit, Bit, Bit)
type ALUFlag = (Bit, Bit)

aluProc :: S ALUCtrl -> S Word -> S Word -> S (Word, ALUFlag)
aluProc c x y =
  zipSY "aluProc" out (zipSY "flagsProc"
                           (tzProc out) (tnProc out))
  where
    (zx,nx,zy,ny,f,no) = unzip6SY "ctrlProc" c
    out = nProc "no" no comp
    comp = compProc f (nProc "nx" nx $ zProc "zx" zx $ x)
                  (nProc "ny" ny $ zProc "zy" zy $ y)
```

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



ForSyDe: Muxes

```
mux2 :: S Bit -> S Word -> S Word -> S Word
mux2 = zipWith3SY "zipWith3SY" $(newProcFun [d]
  f s x y = if s == L then x else y |])
```

```
mux2SysDef :: SysDef (S Bit -> S Word -> S Word -> S Word)
mux2SysDef = newSysDef mux2 "mux2" ["s","i1","i2"] ["o"]
```

```
mux4 :: S (FSVec D2 Bit) -> S (FSVec D4 Word) -> S Word
mux4 ss is = (mux2' "m1") (sv ! d1) m00 m01 where
  mux2' l = instantiate l mux2SysDef
  sv      = unzipxSY "unzipSel" ss
  iv      = unzipxSY "unzipInp" is
  m00     = (mux2' "m00") (sv ! d0) (iv ! d0) (iv ! d1)
  m01     = (mux2' "m01") (sv ! d0) (iv ! d2) (iv ! d3)
```

```
mux4SysDef :: SysDef ( S (FSVec D2 Bit) -> S (FSVec D4 Word)
                      -> S Word)
mux4SysDef = newSysDef mux4 "mux4" ["s","is"] ["o"]
```

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



Universiteit Utrecht

Remarks

Positive:

- ▶ Generated VHDL is very *modular*
 - One VHDL *entity* per ForSyDe component
 - Good for tool integration

Negative:

- ▶ Interface “conflicts” caused by FSVec and process constructors
 - “zip-unzip” pattern

Introduction

Hardware design
Domain-Specific
Languages
Hardware EDSLs

Analyzed EDSLs

Choice criteria
Chosen EDSLs
Evaluation criteria

Modeled Circuits

Choice
ALU
Memory bank
CPU

Analysis of the EDSLs

Lava
ForSyDe
Coquet

Conclusions



ForSyDe: RAM64

```
reg :: S Word -> S Bit -> S Word
reg input load = out where
  out = delaySY "delay" (0 :: WordType) dff
  dff = (instantiate "mux2" mux2SysDef) load out input

ram64 :: S Word -> S (FVec D6 Bit) -> S Bit -> S Word
ram64 input addr load = mux' addr (zipxSY "zipRows" rs) where
  mux'      = instantiate "mux" mux64SysDef
  decoder'  = instantiate "decoder" decode6To64SysDef
  reg' l    = instantiate l regSysDef
  and' l    = instantiate l andSysDef
  r (s,l)   = (reg' l) input ((and' (l ++ ":and")) load s)
  rs'       = unzipxSY "unzipAddr" $ decoder' addr
  rs        = V.map r $ V.zip rs' (V.map (\n -> "r" ++ show n)
                                     (V.unsafeVector d64 [0..63]))

ram64SysDef = newSysDef ram64 "ram64" ["i","a","l"] ["o"]
```

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



Universiteit Utrecht

Remarks

- ▶ Component *instantiation*
 - Introduces *hierarchy* in the design
 - Influences generated VHDL
- ▶ *Manual* name management
 - Error-prone
 - Every process must have a *unique* identifier
 - Already was a (lesser) issue with the muxes

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

Lava
ForSyDe
Coquet

Conclusions



ForSyDe: *Hack* CPU (part)

```
type HackInstruction = FSVec D16 Bit
type Dest = (Bit, Bit, Bit)
type Jump = (Bit, Bit, Bit)

instructionDecoder :: S HackInstruction
                  -> S (Bit, Bit, Dest, Jump, ALUCtrl)
instructionDecoder = mapSY "mapSYdecoder" decoderFun where
  decoderFun = $(newProcFun [d|
    f :: HackInstruction -> (Bit, Bit, Dest, Jump, ALUCtrl)
    f i = ( i!d0
            , not (i!d3)
            , (i!d10, i!d11, i!d12)
            , (i!d13, i!d14, i!d15)
            , (i!d4, i!d5, i!d6, i!d7, i!d8, i!d9)
            ) |])
```

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



The Circuit type

```
Context {tech : Techno}
Inductive Circuit : Type -> Type -> Type :=
| Atom : forall {n m : Type} {Hfn : Fin n} {Hfm : Fin m},
      techno n m -> Circuit n m

| Plug : forall {n m : Type} {Hfn : Fin n} {Hfm : Fin m}
      (f : m -> n), Circuit n m

| Ser : forall {n m p : Type},
      Circuit n m -> Circuit m p -> Circuit n p

| Par : forall {n m p q : Type},
      Circuit n p -> Circuit m q
      -> Circuit (n + m) (p + q)

| Loop : forall {n m p : Type},
      Circuit (n + p) (n + p) -> Circuit n m
```

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



Coquet

```
Definition HADD a b s c: circuit ([:a] + [:b]) ([:s] + [:c]) :=  
  Fork2 ([:a] + [:b])  
  |> (XOR a b s & AND a b c).
```

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



Coquet

```
Program Definition FADD a b cin sum cout :  
  circuit ([:cin] + ([:a] + [:b])) ([:sum] + [:cout]) :=  
  
    (ONE [: cin] & HADD a b "s" "co1")  
|> Rewire (* (a, (b,c)) => ((a,b), c) *)  
|> (HADD cin "s" sum "co2" & ONE [: "co1"])  
|> Rewire (* ((a,b), c) => (a, (b,c)) *)  
|> (ONE [:sum] & OR "co2" "co1" cout).
```

Next Obligation. revert H; plug_def. Defined.

Next Obligation. plug_auto. Defined.

Next Obligation. revert H; plug_def. Defined.

Next Obligation. plug_auto. Defined.

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



Universiteit Utrecht

Coquet: Meaning relation

```
Inductive Sem : forall {n} {m},  
  C n m -> (n -> Data) -> (m -> Data) -> Prop :=  
  
| KAtom: forall n m {Hfn: Fin n} {Hfm: Fin m}  
  (t: techno n m) i o, spec t i o -> Sem (Atom t) i o  
  
| KSer: forall n m p (x: C n m) (y: C m p) i mid o,  
  Sem x i mid -> Sem y mid o -> Sem (Ser x y) i o  
  
| KPar: forall n m p q (x: C n p) (y: C m q) i o,  
  Sem x (select_left i) (select_left o)  
  -> Sem y (select_right i) (select_right o)  
  -> Sem (Par x y) i o  
  
| KPlug: forall n m {Hfn: Fin n} {Hfm: Fin m} (f: m -> n) i,  
  Sem (Plug f) i (Data.lift f i)  
  
| KLoop: forall n m l (x: C (n + l) (m + l)) i o ret,  
  Sem x (Data.app i ret) (Data.app o ret)  
  -> Sem (Loop x) i o
```

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



Coquet: Specification

```
Context {n m N M : Type}
  (Rn : Iso (n -> T) N) (Rm : Iso (m -> T) M).

Class Realise (c : Circuit n m) (R : N -> M -> Prop) :=
  realise: forall i o, Semantics c i o -> R (iso i) (iso o)

Class Implement (c : Circuit n m) (f : N -> M) :=
  implement: forall i o, Semantics c i o -> iso o = f (iso i)
```

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



Coquet: Correctness proofs

```
Instance HADD_Implement {a b s c} :  
  Implement (HADD a b s c) _ _  
    (fun (x : bool * bool) =>  
      match x with (a,b) => (xorb a b, andb a b) end).  
Proof.  
  unfold HADD; intros ins outs H; tac.  
Qed.
```

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet**

Conclusions



Coquet: How to prove correctness

```
Ltac tac :=  
  rinvert; (* destruct the circuit *)  
  realise_all; (* use the hint data-base *)  
  unreify_all bool; (* unreify *)  
  destruct_all; (* destruct the booleans *)  
  intros_all;  
  clear;  
  boolean_eq.
```

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet**

Conclusions



Section 5

Conclusions

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



Results

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



Future work

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions



Thank you!

Questions?

