

Comparing functional Embedded Domain-Specific Languages for hardware description

João Paulo Pizani Flor

Department of Information and Computing Sciences, Utrecht University

February 13th, 2014

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

Lava
ForSyDe
Coquet

Conclusions

Results
Future work



Universiteit Utrecht

Section 1

Introduction

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions

- Results
- Future work



Hardware design

Introduction

Hardware design

- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions

- Results
- Future work



Domain-Specific Languages

A computer language (turing-complete or *not*) targeting a *specific application domain*.

Example DSLs:

- ▶ SQL (database queries)
- ▶ CSS (document formatting)
- ▶ MATLAB (Matrix programming)
- ▶ VHDL (Hardware description)

Introduction

Hardware design
Domain-Specific
Languages
Hardware EDSLs

Analyzed EDSLs

Choice criteria
Chosen EDSLs
Evaluation criteria

Modeled Circuits

Choice
ALU
Memory bank
CPU

Analysis of the EDSLs

Lava
ForSyDe
Coquet

Conclusions

Results
Future work



Domain-Specific Languages

A computer language (turing-complete or *not*) targeting a *specific application domain*.

Example DSLs:

- ▶ SQL (database queries)
- ▶ CSS (document formatting)
- ▶ MATLAB (Matrix programming)
- ▶ VHDL (Hardware description)

A DSL can also be *embedded* in a general-purpose language.

Example EDSLs:

- ▶ Boost.Proto (C++ / parser combinators)
- ▶ Diagrams (Haskell / programmatic drawing)
- ▶ Parsec (Haskell / parser combinators)

Introduction

Hardware design
Domain-Specific
Languages
Hardware EDSLs

Analyzed EDSLs

Choice criteria
Chosen EDSLs
Evaluation criteria

Modeled Circuits

Choice
ALU
Memory bank
CPU

Analysis of the EDSLs

Lava
ForSyDe
Coquet

Conclusions

Results
Future work



Example of an EDSL: Parsec

A simple parser for a "Game of Life"-like input format:

```
dead, alive :: Parser Bool
dead  = fmap (const False) (char '.')
alive = fmap (const True) (char '*')

line :: Parser [Bool]
line  = many1 (dead <|> alive)

board :: Parser [[Bool]]
board = line 'endBy1' newline

parseBoardFromFile :: FilePath -> IO [[Bool]]
parseBoardFromFile filename = do
  result <- parseFromFile board filename
  return $ either (error . show) id result
```

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions

- Results
- Future work



Example of a hardware EDSL

Some Lava code. . .

Introduction

- Hardware design
- Domain-Specific Languages

Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions

- Results
- Future work



Section 2

Analyzed EDSLs

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions

- Results
- Future work



Choice criteria

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

Choice criteria

- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions

- Results
- Future work



Chosen EDSLs

The language we chose to evaluate, with the respective host language, were:

- ▶ Lava (Haskell - *chalmers-lava dialect*)
- ▶ ForSyDe (Haskell)
- ▶ Coquet (Coq)

Introduction

Hardware design
Domain-Specific
Languages
Hardware EDSLs

Analyzed EDSLs

Choice criteria
Chosen EDSLs
Evaluation criteria

Modeled Circuits

Choice
ALU
Memory bank
CPU

Analysis of the EDSLs

Lava
ForSyDe
Coquet

Conclusions

Results
Future work



Section 3

Modeled Circuits

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions

- Results
- Future work



Chosen circuits

We cherry-picked circuits from the book “Elements of Computing Systems”, as they satisfied all of our demands.

 


Figure: “Elements of Computing Systems” - Nisan, Schocken, available at <http://www.nand2tetris.org>.

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

Choice

- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions

- Results
- Future work



Universiteit Utrecht

Chosen circuits

Circuit 1 A 2-input, 16-bit-wide, simple ALU

Circuit 2 A 64-word long, 16-bit wide memory block

Circuit 3 An *extremely* reduced instruction set CPU, the *Hack* CPU.

Let's take a quick look at each of these circuit's specification. . .

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions

- Results
- Future work



Circuit 1: block diagram

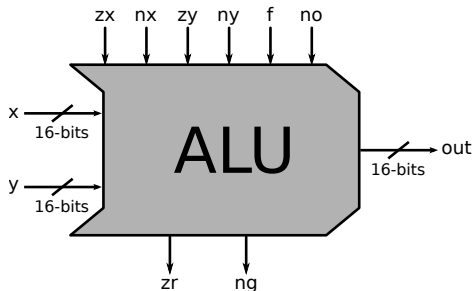


Figure: Input/Output ports of *circuit 1*, the ALU.

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions

- Results
- Future work



Universiteit Utrecht

Circuit 1: specification

The behaviour of the ALU is specified by the values of the *control bits* and *flags*:

zx and zy Zeroes the “x” and “y” inputs, respectively

nx and ny *bitwise negation* on the “x” and “y” inputs

f Selects the function to be applied:

“f” = 1 for addition, “f” = 0 for bitwise AND

no *bitwise negation* on the output ALU output

zr and ng The output *flag* “zr” = 1 *iff* the ALU output is zero. “ng” = 1 *iff* the output is negative.

Operations such as bitwise OR, subtraction, etc. can be done by setting the control bits appropriately.

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions

- Results
- Future work



Circuit 2: RAM64

Some of the circuit's key characteristics:

- ▶ *Sequential* circuit, with clock input
- ▶ 64 memory words stored, each 16-bit wide
- ▶ Address port has width $\log_2 64 = 16$ bit

Introduction

Hardware design
Domain-Specific
Languages
Hardware EDSLs

Analyzed EDSLs

Choice criteria
Chosen EDSLs
Evaluation criteria

Modeled Circuits

Choice
ALU
Memory bank
CPU

Analysis of the EDSLs

Lava
ForSyDe
Coquet

Conclusions

Results
Future work



Circuit 2: block diagram

 


Figure: Input/Output ports of *circuit 2*, the RAM64 block.

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions

- Results
- Future work



Circuit 2: specification

The output “out” holds the value at the memory line indicated by “address”.

- ▶ *Iff* “load” = 1, then the value at input “in” will be loaded into memory line “address”.
- ▶ The loaded value will be emitted on “out” at the *next* clock cycle.

Introduction

Hardware design
Domain-Specific
Languages
Hardware EDSLs

Analyzed EDSLs

Choice criteria
Chosen EDSLs
Evaluation criteria

Modeled Circuits

Choice
ALU
Memory bank
CPU

Analysis of the EDSLs

Lava
ForSyDe
Coquet

Conclusions

Results
Future work



Circuit 3: block diagram

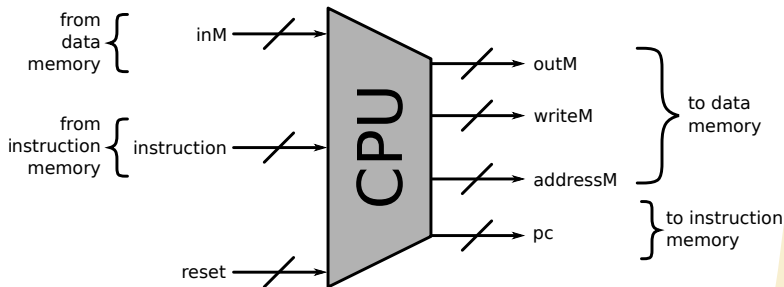


Figure: Input/Output ports of *circuit 3*, the *Hack CPU*.

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions


- Results
- Future work



Circuit 3: specification

Circuit 3 runs “A” and “C” instructions, according to the *Hack assembly specification*.

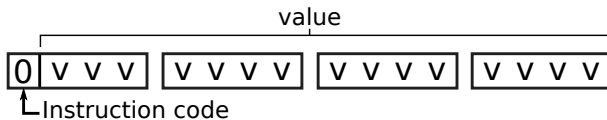- ▶ The “A” instruction: sets the “A” register.



- ▶ The value in “A” can be used:
 - As operand for a subsequent computation
 - As address for jumps

Introduction

Hardware design
Domain-Specific
Languages
Hardware EDSLs

Analyzed EDSLs

Choice criteria
Chosen EDSLs
Evaluation criteria

Modeled Circuits

Choice
ALU
Memory bank
CPU

Analysis of the EDSLs

Lava
ForSyDe
Coquet

Conclusions


Results
Future work



Circuit 3: specification

Circuit 3 runs “A” and “C” instructions, according to the *Hack assembly specification*.

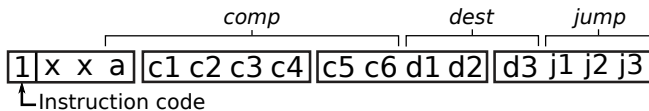- ▶ The “C” instruction: sets the “C” register, performs *computation* or *jumps*.



- ▶ Some peculiarities:
 - Bits “c1” to “c6” control the ALU
 - *conditional* or *unconditional* jumps
 - *destination* of the computation result: “A”, “D”, “M”

Introduction

Hardware design
Domain-Specific
Languages
Hardware EDSLs

Analyzed EDSLs

Choice criteria
Chosen EDSLs
Evaluation criteria

Modeled Circuits

Choice
ALU
Memory bank
CPU

Analysis of the EDSLs

Lava
ForSyDe
Coquet

Conclusions

Results
Future work



Circuit 3: specification (parts)

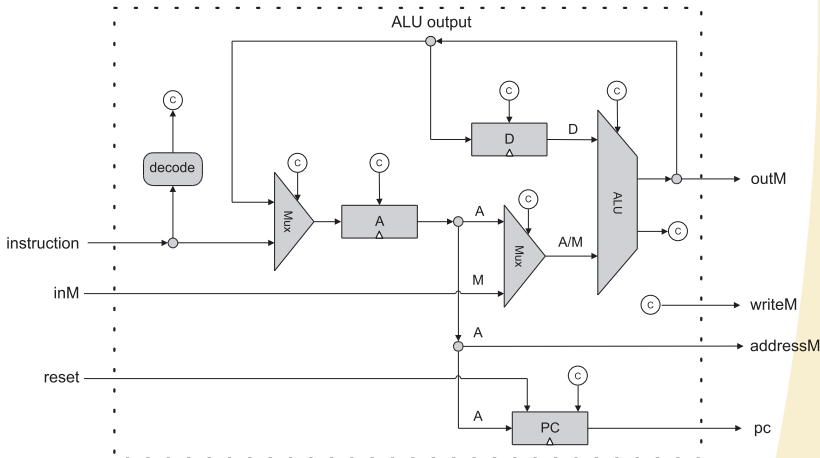


Figure: Parts used to build the *Hack* CPU, and their interconnection.

Introduction

Hardware design
Domain-Specific
Languages
Hardware EDSLs

Analyzed EDSLs

Choice criteria
Chosen EDSLs
Evaluation criteria

Modeled Circuits

Choice
ALU
Memory bank
CPU

Analysis of the EDSLs

Lava
ForSyDe
Coquet

Conclusions

Results
Future work



Section 4

Analysis of the EDSLs

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions

- Results
- Future work



Lava

```
type SB = Signal Bool

halfAdder :: (SB, SB) -> (SB, SB)
halfAdder inputs = (xor2 inputs, and2 inputs)

fullAdder :: (SB, (SB, SB)) -> (SB, SB)
fullAdder (cin, (a, b)) = (s, cout)
  where
    (ab, c1) = halfAdder (a, b)
    (s, c2)  = halfAdder (ab, cin)
    cout    = or2 (c1, c2)

rippleCarryAdder :: [(SB, SB)] -> [SB]
rippleCarryAdder ab = s
  where (s, _) = row fullAdder (low, ab)
```

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions

- Results
- Future work



```
type ALUControlBits = (SB, SB, SB, SB, SB, SB)

alu :: ([SB], [SB], ALUControlBits) -> ([SB], SB, SB)
alu (x, y, (zx, nx, zy, ny, f, no)) = (out', zr, ng)
  where x'      = mux (zx, (x, replicate (length x) low))
        x''     = mux (nx, (x', map inv x'))
        y'      = mux (zy, (y, replicate (length x) low))
        y''     = mux (ny, (y', map inv y'))
        out     = let xy'' = zip x'' y''
                  in mux (f, (and1 xy'', adder xy''))
        out'    = mux (no, (out, map inv out))
        zr      = foldl (curry and2) low out'
        ng      = equalBool high (last out')
        adder   = rippleCarryAdder
```

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions

- Results
- Future work



```
prop_FullAdderCommutative :: (SB, (SB, SB)) -> Signal Bool
prop_FullAdderCommutative (c, (a, b)) =
    fullAdder (c, (a, b)) <==> fullAdder (c, (b, a))
```

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

Lava

- ForSyDe
- Coquet

Conclusions

- Results
- Future work



ForSyDe: ALU

```
bo = bitToBool
bb = boolToBit

aluFunc :: ProcFunc (ALUControl -> WordType -> WordType
                    -> (WordType, ALUFlags))

aluFunc = $(newProcFun [d|
  aluFunc' (zx,nx,zy,ny,f,no) x y =
    ( out,  (bb (out == 0), bb (out < 0)) )
  where
    zf z w  = if bo z then 0 else w
    nf n w  = if bo n then complement w else w
    (xn, yn) = (nf nx $ zf zx $ x,  nf ny $ zf zy $ y)
    out     = nf no $ case f of
                        ALUSum -> xn + yn
                        ALUAnd -> xn .&. yn  |] )
```

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions

- Results
- Future work



ForSyDe: Muxes

```
type S a = Signal a
type WT = WordType
```

```
mux2 :: S Bit -> S WT -> S WT -> S WT
mux2 = zipWith3SY "zipWith3SY" $(newProcFun [d]
  f s x y = if s == L then x else y [])
```

```
mux2SysDef :: SysDef (S Bit -> S WT -> S WT -> S WT)
mux2SysDef = newSysDef mux2 "mux2Sys"
  ["sel", "in1", "in2"] ["out"]
```

```
mux4 :: S (FSVec D2 Bit) -> S (FSVec D4 WT) -> S WT
mux4 ss is = (mux2' "m1") (sv ! d1) m00 m01 where
  mux2' l = instantiate l mux2SysDef
  sv      = unzipxSY "unzipSel" ss
  iv      = unzipxSY "unzipInp" is
  m00     = (mux2' "m00") (sv ! d0) (iv ! d0) (iv ! d1)
  m01     = (mux2' "m01") (sv ! d0) (iv ! d2) (iv ! d3)
```

```
mux4SysDef :: SysDef (S (FSVec D2 Bit) -> S (FSVec D4 WT) -> S WT)
mux4SysDef = newSysDef mux4 "mux4Sys"
  ["sel", "inputs"] ["out"]
```

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions

- Results
- Future work



The Circuit type

```
Context {tech : Techno}
Inductive Circuit : Type -> Type -> Type :=
| Atom : forall {n m : Type} {Hfn : Fin n} {Hfm : Fin m},
      techno n m -> Circuit n m

| Plug : forall {n m : Type} {Hfn : Fin n} {Hfm : Fin m}
      (f : m -> n), Circuit n m

| Ser : forall {n m p : Type},
      Circuit n m -> Circuit m p -> Circuit n p

| Par : forall {n m p q : Type},
      Circuit n p -> Circuit m q
      -> Circuit (n + m) (p + q)

| Loop : forall {n m p : Type},
      Circuit (n + p) (n + p) -> Circuit n m
```

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions

- Results
- Future work



Coquet

```
Definition HADD a b s c: circuit ([:a] + [:b]) ([:s] + [:c]) :=  
  Fork2 ([:a] + [:b])  
  |> (XOR a b s & AND a b c).
```

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet**

Conclusions

- Results
- Future work



```
Program Definition FADD a b cin sum cout :  
  circuit ([:cin] + ([:a] + [:b])) ([:sum] + [:cout]) :=  
  
    (ONE [: cin] & HADD a b "s" "co1")  
|> Rewire (* (a, (b,c)) => ((a,b), c) *)  
|> (HADD cin "s" sum "co2" & ONE [: "co1"])  
|> Rewire (* ((a,b), c) => (a, (b,c)) *)  
|> (ONE [:sum] & OR "co2" "co1" cout).
```

Next Obligation. revert H; plug_def. Defined.

Next Obligation. plug_auto. Defined.

Next Obligation. revert H; plug_def. Defined.

Next Obligation. plug_auto. Defined.

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions

- Results
- Future work



Section 5

Conclusions

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions

- Results
- Future work



Results

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions

- Results**
- Future work



Future work

Introduction

- Hardware design
- Domain-Specific Languages
- Hardware EDSLs

Analyzed EDSLs

- Choice criteria
- Chosen EDSLs
- Evaluation criteria

Modeled Circuits

- Choice
- ALU
- Memory bank
- CPU

Analysis of the EDSLs

- Lava
- ForSyDe
- Coquet

Conclusions

- Results
- Future work



Thank you!

Questions?

